



UNIVERSITI KUALA LUMPUR

---

**FINAL EXAMINATION**  
**JANUARY 2016 SEMESTER**

---

**SUBJECT CODE** : IED11102  
**SUBJECT TITLE** : INTRODUCTION TO ELECTRONICS  
**LEVEL** : DIPLOMA  
**TIME / DURATION** : 3.00 pm – 5.30 pm  
( 2 ½ HOURS )  
**DATE** : 20 MAY 2016

---

**INSTRUCTIONS TO CANDIDATES**

---

1. Please read the instructions given in the question paper CAREFULLY.
2. This question paper is printed on both sides of the paper.
3. This question paper consists of TWO (2) Sections. Section A and B.
4. Answer ALL questions in Section A. For Section B, answer TWO (2) questions only.
5. Please write your answers on the answer booklet provided.
6. Required formula is appended.
7. Answer all questions in English.

---

THERE ARE 6 PAGES OF QUESTIONS, EXCLUDING THIS PAGE AND APPENDIX.

---

**SECTION A (Total: 60 marks)**

**INSTRUCTION: Answer ALL questions.**  
**Please use the answer booklet provided.**

**Question 1**

- (a) Materials can be classified into three groups. What are the three groups? (3 marks)
- (b) What is the difference between intrinsic and extrinsic semiconductors? (4 marks)
- (c) What is the difference between a pentavalent atom and a trivalent atom? What are other names for these atoms? (4 marks)
- (d) With the aid of diagrams, explain the difference between insulator, semiconductor and conductor in terms of its atomic structure. Give an example of each material. (9 marks)

**Question 2**

- (a) What is the barrier potential for a germanium diode? (2 marks)
- (b) What is the output voltage that you would expect to observe across  $R_L$  in the clamping circuit of Figure 1? Assume that  $RC$  is large enough to prevent significant capacitor discharge.

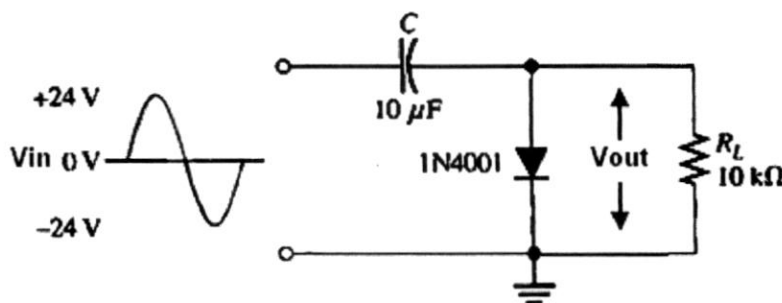


Figure 1

(4 marks)

- (c) For the series diode configuration of Figure 2, determine  $V_D$ ,  $V_R$  and  $I_D$ .

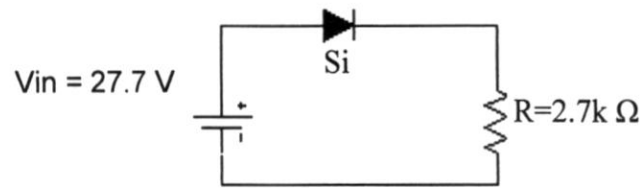


Figure 2

(6 marks)

- (d) With the aid of diagrams, explain the operation of semiconductor diode under forward and reverse biased conditions.

(8 marks)

### Question 3

- (a) What is the main difference between BJT and FET? (2 marks)
- (b) What are the two main applications of BJT? (2 marks)
- (c) Determine the value of  $I_E$  and  $\alpha_{dc}$  of a transistor, if  $I_C = 5.34\text{mA}$  and  $I_B = 475\mu\text{A}$ . (4 marks)
- (d) Calculate the value of  $\beta_{DC}$  for a transistor, if  $I_E = 20.5\text{mA}$  and  $I_C = 20.3\text{mA}$ . (4 marks)
- (e) In a certain transistor circuit, the base current is 2 percent of the 30mA emitter current. Determine the value of  $I_C$ ,  $\beta_{dc}$  and  $\alpha_{dc}$ .

(8 marks)

SECTION B (Total: 40 marks)

INSTRUCTION: Answer TWO (2) questions only.

Please use the answer booklet provided.

Question 4

- (a) Determine the peak value of the output voltage for Figure 3 if the turns ratio is 0.5.

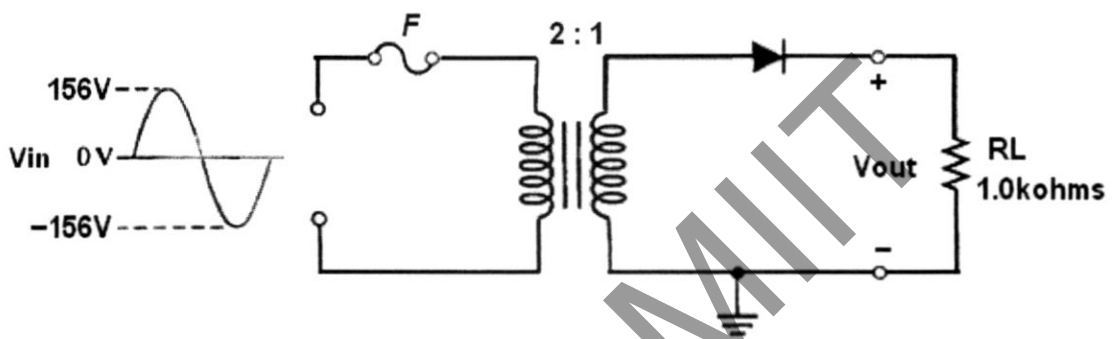


Figure 3

(4 marks)

- (b) For the full-wave rectified voltage in Figure 4, determine;

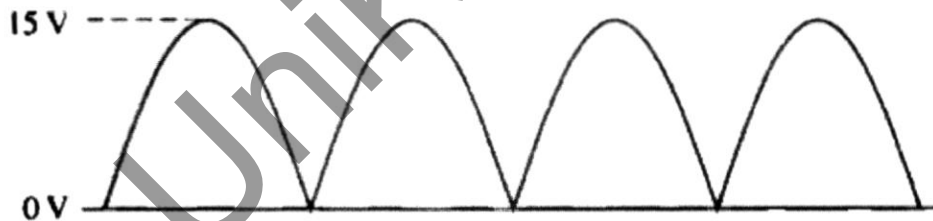


Figure 4

- i. Peak Rectified Voltage,  $V_{PR}$ .

(2 marks)

- ii. Average value,  $V_{avg}$ .

(2 marks)

- ii. RMS value,  $V_{rms}$

(2 marks)

- (c) i. Show the voltage waveform across each half of the secondary winding and across RL when a 240V peak sine wave is applied to the primary winding in Figure 5.

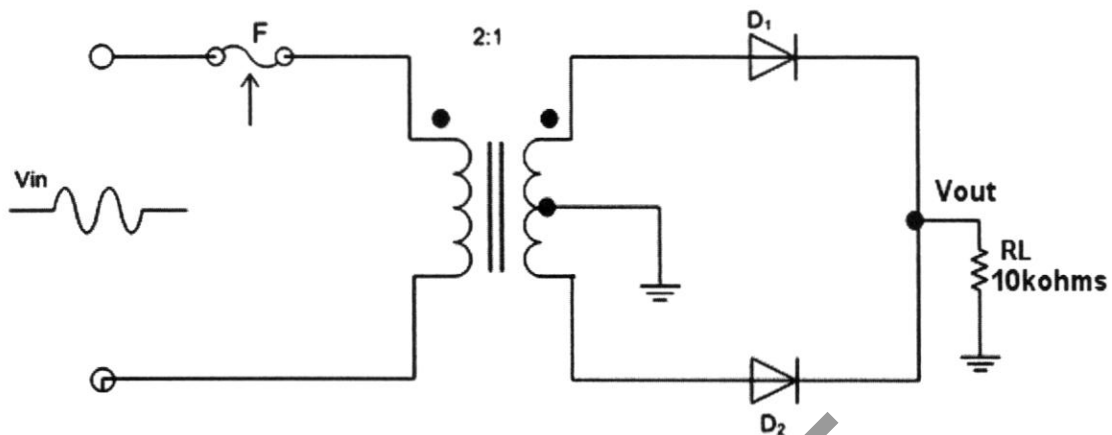


Figure 5

- (8 marks)
- ii. Calculate the minimum PIV rating for the diode. (2 marks)

**Question 5**

- (a) A certain amplifier exhibits an output power of 5W with an input power of 0.5W. Determine the value of power gain in dB. (2 marks)
- (b) If the output voltage of an amplifier is 1.2V rms and its voltage gain is 50, what is the rms input voltage? Calculate the value of voltage gain in dB. (4 marks)
- (c) Suppose that an amplifier has a voltage gain of 50, an input resistance of 1kΩ and an output resistance of 150Ω. Determine the value of  $A_V$  and  $A_P$  in dB? (6 marks)

(d) For the circuit in Figure 6, given  $r_{e'} = 50\Omega$  and  $\beta = 200$ .

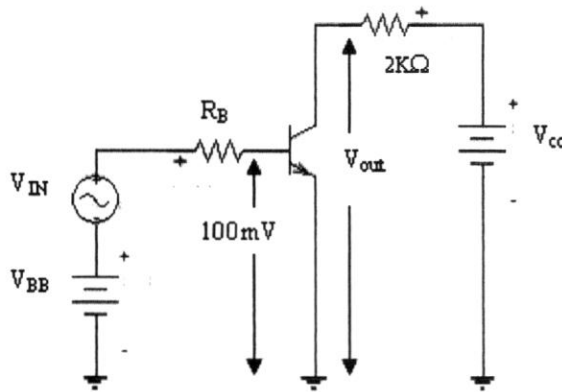


Figure 6

Determine;

- i. The current gain ( $A_i$ ) (2 marks)
- ii. The voltage gain ( $A_v$ ) (2 marks)
- iii. The ac output voltage ( $V_{OUT}$ ) (2 marks)
- iv. The power gain ( $A_p$ ) in dB (2 marks)

**Question 6**

(a) A base current of  $50\mu A$  is applied to the transistor in Figure 7, and a voltage of 5 V is dropped across  $R_c$ . Determine  $\beta_{DC}$  of the transistor.

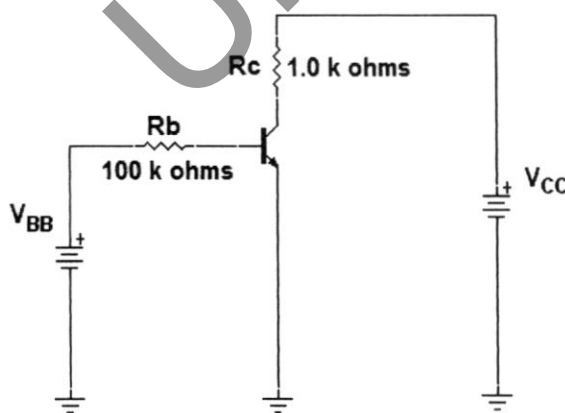


Figure 7

(6 marks)

- (b) Design a biased-transistor circuit using  $V_{BB} = 10V$  and  $V_{CC} = 20V$ , for a Q point of  $I_B = 5mA$  and  $V_{CE} = 4V$ . Given  $\beta_{DC} = 100$ . The design should determine the  $R_B$  and  $R_C$ . Sketch the circuit.

(6 marks)

- (c) For the transistor circuit in Figure 8, calculate  $I_B$ ,  $I_C$ ,  $I_E$ ,  $V_{CE}$  where  $\beta_{dc} = 80$ ,  $V_B = 2V$  and  $V_E = 1.3V$ .

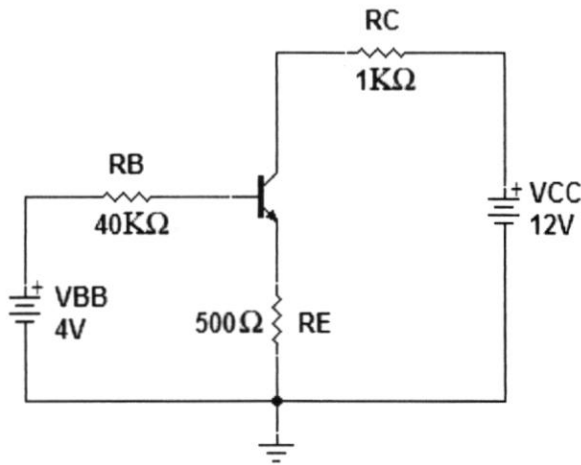


Figure 8

(8 marks)

END OF EXAMINATION PAPER

## APPENDIX

## Formula Sheet

$$1. \quad \beta = \frac{\alpha}{1 - \alpha}$$

$$2. \quad \alpha = \frac{\beta}{1 + \beta}$$

$$3. \quad I_E = I_B + I_C$$

$$4. \quad I_C = \beta I_B$$

$$5. \quad P = [V_{DC} - V_{load}] I_{out}$$

$$6. \quad \theta_{JA(max)} = \frac{J_{JA(max)} - T_A}{P}$$

$$7. \quad V_{rippleout(p-p)} = V_{ripplein(p-p)} \times 10^{-[(dB - 20 \log V_{out})/20]}$$

$$8. \quad V_B = \frac{R_{B2} \times V_{CC}}{R_{B1} + R_{B2}}$$

$$9. \quad V_E = V_B - 0.7$$

$$10. \quad I_E = \frac{V_E}{R_E}$$

$$11. \quad I_C \approx I_E$$

$$12. \quad V_{RC} = I_C R_C$$

$$13. \quad V_{CE} = V_{CC} - V_{RC} - V_E$$

$$14. \quad V_C = V_{CC} - I_C R_C$$