

**UNIVERSITI KUALA LUMPUR
MALAYSIAN INSTITUTE OF INDUSTRIAL TECHNOLOGY**

**FINAL EXAMINATION
JANUARY 2016 SEMESTER**

COURSE CODE : JCB 10503
COURSE TITLE : ANALOG ELECTRONICS
PROGRAMME LEVEL : BACHELOR
DATE : 30 MAY 2016
TIME : 9.00 AM – 12.00 PM
DURATION : 3 HOURS

INSTRUCTIONS TO CANDIDATES

- 1. Please read the instructions given in the question paper CAREFULLY.**
- 2. This question paper is printed on both sides of the paper.**
- 3. This question paper consists of ONE (1) section.**
- 4. Answer FIVE (5) questions ONLY in Section A.**
- 5. Please write your answers on the answer booklet provided.**
- 6. Please answer all questions in English only.**

THERE ARE 7 PAGES OF QUESTIONS EXCLUDING THIS PAGE.

SECTION A (Total: 100 marks)

INSTRUCTION: Answer FIVE (5) questions ONLY.

Please use the answer booklet provided.

Question 1

- (a) With the aid of suitable diagram, discuss **TWO (2)** characteristics of conductor and insulator.

(6 marks)

- (b) A 2V stabilized power supply is required to be produced from a 20V DC power supply input source. The maximum power rating, P_Z of the zener diode is 2.3W. Using the following zener regulator circuit, solve:

 


Figure 1: Zener regulator circuit.

- (i) The maximum current flowing through the zener diode. (2 marks)
- (ii) The minimum value of the series resistor, R_s . (2 marks)
- (iii) The load current I_L if a load resistor of $1\text{k}\Omega$ is connected across the zener diode. (2 marks)
- (iv) The zener current I_z at full load. (2 marks)

- (c) Examine the input and output waveform of a rectifier circuit as shown in Figure 2. Classify the type of the rectifier. Then, design the required rectifier circuit using ideal diodes.

(6 marks)

 


Figure 2: Input and output waveform of rectifier circuit.

Question 2

- (a) With the aid of suitable diagram, differentiate **TWO (2)** characteristics between common base and common emitter configurations.

(6 marks)

- (b) From Figure 3, prove that the base current, $I_B = \frac{V_{CC} - V_{BE}}{R_B}$ and collector-to-emitter voltage, $V_{CE} = V_{CC} - I_C R_C$. Illustrate the input and output loop circuit.

(6 marks)

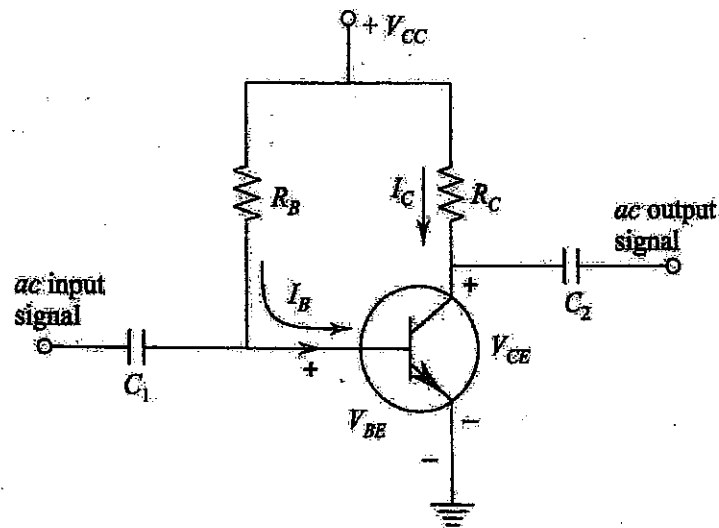


Figure 3: Fixed-bias circuit of a transistor.

- (c) Using the same fixed-bias circuit in part b and given the values of $V_{CC} = 25V$, $R_B = 205k\Omega$, $R_C = 1.2k\Omega$, $\beta = 100$, determine:

- (i) Base current, I_B . (2 marks)

- (ii) Collector current, I_C . (2 marks)

- (iii) Collector-to-emitter voltage, V_{CE} . (2 marks)

- (iv) Base voltage, V_B . (2 marks)

Question 3

- (a) Compare **FOUR (4)** characteristics of bipolar junction transistor (BJT) and field-effect transistor (FET). (4 marks)
- (b) Given the value of maximum drain saturation current, $I_{DSS} = 5 \text{ mA}$ and peak voltage, $V_p = -4 \text{ V}$. For the self-bias configuration of Figure 4, determine:

 


Figure 4: Self bias configuration circuit.

- | | |
|---|-----------|
| (i) Gate to source voltage, V_{GSQ} . | (8 marks) |
| (ii) Drain current, I_{DQ} . | (1 mark) |
| (iii) Drain to source voltage, V_{DS} . | (2 marks) |
| (iv) Source voltage, V_s . | (2 marks) |
| (v) Gate voltage, V_G . | (1 mark) |
| (vi) Drain voltage, V_D . | (2 marks) |

Question 4

(a) Explain **FOUR (4)** characteristics of a good amplifier.

(4 marks)

(b) Figure 5 illustrates the BJT amplifier circuit. Given the parameters of the amplifier is

$\beta = 100$, $r_{bb'} = 20\Omega$, $r_{ce} = 20\Omega$ and $V_{BE} = 0.7V$. From the figure,

 


Figure 5: BJT amplifier circuit.

(i) Predict the types of BJT configuration for the amplifier circuit.

(2 marks)

(ii) Design the AC equivalent amplifier circuit using hybrid- π model.

(5 marks)

(iii) Examine emitter current, I_E and r_e .

(5 marks)

(iv) Examine input and output impedances, Z_i and Z_o .

(2 marks)

(v) Examine voltage and current gain, A_v and A_i .

(2 marks)

Question 5

- (a) With the aid of suitable diagram, explain a concept of positive and negative feedbacks. (6 marks)
- (b) Figure 6 shows an output of a periodic waveform of a 555 timer. To generate the periodic waveform,

 


Figure 6: An output of a periodic waveform of 555 timer.

- (i) Design a circuit using the 555 timer. Use capacitor values of $0.01 \mu\text{F}$. Draw and label the 555 timer. (6 marks)
- (ii) Modify the circuit in part (i) to give a duty cycle of 20% without changing the value of the frequency. Draw and label the modified 555 timer circuit. Then, interpret the operation of the circuit. (8 marks)

Question 6

- (a) Figure 7 illustrates a basic connection of operational amplifier (op-amp) circuit. By applying an ideal op-amp characteristics, design the op-amp AC equivalent circuit. Draw and label the equivalent circuit.

(6 marks)



 


Figure 7: Basic connection of operational amplifier circuit.

 - (b) Figure 8 shows a differential and common-mode operation for an operational amplifier. Solve:



(a) Differential operation

 

(b) Common-mode operation

Figure 8: Operational amplifier circuits.

- (i) Differential input voltage, V_d . Draw the equivalent circuit for the differential operation. (4 marks)
- (ii) Common input voltage, V_c . Draw the equivalent circuit for the common-mode operation. (4 marks)
- (iii) Common-mode rejection ratio, CMRR. (6 marks)

END OF EXAMINATION PAPER