



UNIVERSITI KUALA LUMPUR
MALAYSIAN INSTITUTE OF MARINE ENGINEERING TECHNOLOGY

FINAL EXAMINATION
SEPTEMBER 2016 SEMESTER

COURSE CODE	: LEB30103
COURSE NAME	: POWER ELECTRONICS
PROGRAMME NAME (FOR MPU: PROGRAMME LEVEL)	: BACHELOR OF ENGINEERING TECHNOLOGY IN MARINE ELECTRICAL AND ELECTRONICS
DATE	: 16TH JANUARY 2016
TIME	: 02.00 PM – 05.00 PM
DURATION	: 3 HOURS


INSTRUCTIONS TO CANDIDATES

1. Please **CAREFULLY** read the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **TWO (2)** sections; Section A and Section B.
4. Answer **ALL** questions in Section A. For Section B, answer **TWO (2)** questions.
5. Please write your answers on the answer booklet provided.
6. Answer all questions in English language **ONLY**.

THERE ARE 10 PAGES OF QUESTIONS, INCLUDING THIS PAGE.

PART A (Total: 40 marks)**INSTRUCTION: Answer ALL questions.****Please use the answer booklet provided.****Question 1 (CLO1)**

- a. Explain about the gate drivers and their importance to Power Electronics [5 marks]
- b. Determine the parameters need to be consider, while selecting IGBT. [4 marks]
- c. Explain about the snubber circuit. List of two (2) of their examples. [5 marks]
- d. Converters are classified by the relationship between input and output as shown in **Figure 1**. State the four basic types of power converter, provide names in common usage and briefly explain their examples respectively.

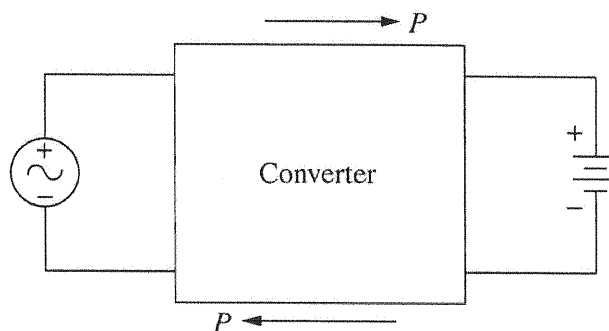**Figure 1**

[6 marks]

Question 2 (CLO 2)

- a. Sketch the waveform for the circuit shown in Figure 2 below by using **APPENDIX 1**.

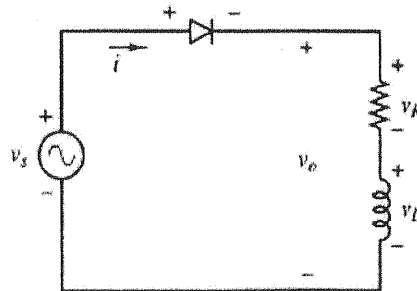


Figure 2

[7 marks]

- b. The operational conditions for the fully controlled AC-to-DC converter shown in Figure 3 below and given in table 1.

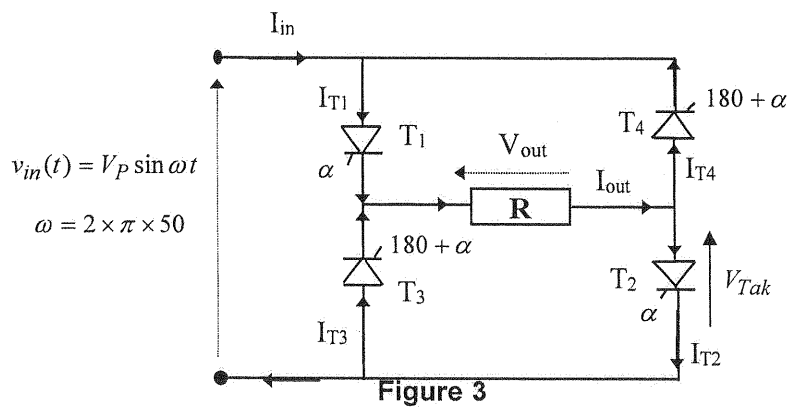


Figure 3

Table 1

$V_{in,rms}$	R	α
240	20Ω	40°

- (i) Explain briefly the operation of single phase full-wave controlled rectifier with R load as shown in Figure 3.

[3 marks]

- (ii) Refer figure 3, determine using **APPENDICES 2,3 and 4** as appropriate:

- The SCR rms current rating required [2 marks]
- The output power [3 marks]
- The input power factor [1 mark]
- The input volt-amperes [2 marks]
- Determine the input line 3rd Harmonic rms current [2 marks]


PART B (Total: 60 marks)**INSTRUCTION: Answer only THREE (3) questions.****Please use the answer booklet provided.****Question 3 (CLO 5)**

- a. Show that average output voltage of a DC-to-DC boost converter is given by expression:

$$V_o(av) = \frac{V_s}{(1-D)}$$

Where V_s is the dc source voltage and D is the duty cycle. Prove the equation above.

[6 marks]

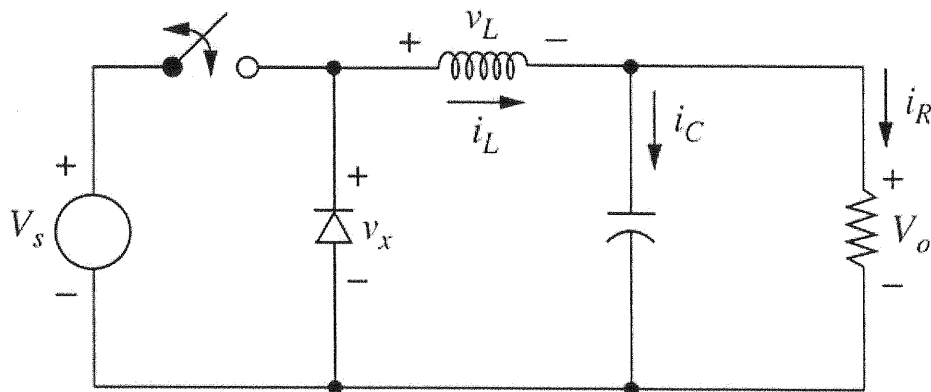**Figure 4**

- b. The buck converter of **Figure 4** has an input of 50 V and the output of 25 V. The switching frequency is 100 kHz, and the output power to a load resistor 125 W.
- Determine the duty ratio. [2 marks]
 - Determine the value of inductance to limit the peak inductor current to 6.25 A [4 marks]
 - Determine the value of capacitance to limit the output voltage ripple to 0.5%. [3 marks]
 - Sketch the graph for maximum and minimum inductor current [3 marks]
 - Sketch the graph output voltage for this DC buck converter and include the value output voltage ripple. [2 marks]

Question 4 (CLO 3)

The Figure 5 shows the switching patterns for amplitude and harmonic control of the full bridge inverter with the dc source is 125 V, the load is a series RL connection with $R = 10$ and $L = 20$ mH, and the switching frequency is 60 Hz. By referring to

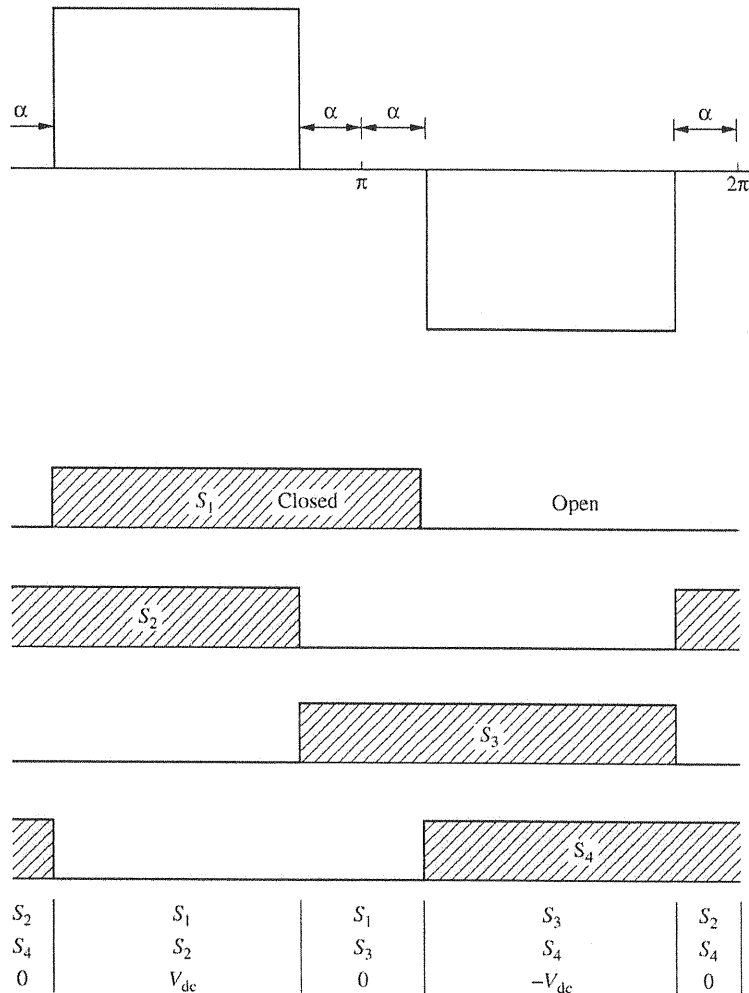


Figure 5

- i. Determine the value of α to produce an output with an amplitude of 90 V at the fundamental frequency. [4 marks]
- ii. Determine the THD of the load current [7 marks]
- iii. Explain three (3) reasons why need to consider harmonics [3 marks]

- b. **Table 2** below shows the reading for Fourier series quantities taken from harmonics waveform. Analyze total Harmonic Distortion for current (THDi) and total Harmonic Distortion for voltage (THDv)

Table 2

n	f(Hz)	V_n(V)	Z_n(Ω)	I_n(A)
1	60	127	13.7	9.27
3	180	0	30	0
5	300	25.5	48.2	0.53
7	420	18.2	66.7	0.27
9	540	0	85.4	0
11	660	11.6	104	0.11

[6 marks]

Question 5 (CLO 4)

- a. List of two (2) ways operating modes of DC Motor in variable speed drive (VSD) applications. Discuss briefly **regenerative braking** operating mode operation.

[3 marks]

- b. Consider a 500V, 10kW, 20A rated-DC Motor with armature resistance of $R_a = 1\Omega$ when supplied at 500V, the unloaded motor runs at 1040rev/min, drawing a current of 0.8A.

- (i) Estimate the full load speed at rated values

[2 marks]

- (ii) Estimate the no-load speed at 250V

[2 marks]

- c. The speed of a separately excited DC Motor is controlled by a single phase full wave converter at armature side. The field circuit is controlled by a single phase semi-converter that is set to maximum possible value. The ac supply to the armature and field converters in one phase, 230V, 50Hz. The armature resistance, $R_a = 0.25\Omega$, field resistance, $R_f = 140\Omega$ and the motor voltage constant is $K_v = 1.125V / A / rad / s$. The load torque is $T_L = 60N.m$ at 1000rpm. The friction and no load losses are negligible. The inductance of the armature and field current continuous and ripple free. Determine:

- (i) The motor Back EMF, E_g

[4 marks]

- (ii) The delay angle of the converter in the armature circuit, α_a

[4 marks]

- (iii) If the load torque, T_L decrease to 45N.m at 1100rpm, calculate (i) and (ii)

[5 marks]

QUESTION 6

- a. The full-bridge resonant inverter of **Figure 6** has a $8\ \Omega$ resistive load that requires a 1200-Hz, 100-V rms sinusoidal voltage. The THD of the load voltage must be no more than 10 percent. Determine the required dc input and suitable values for L and C .

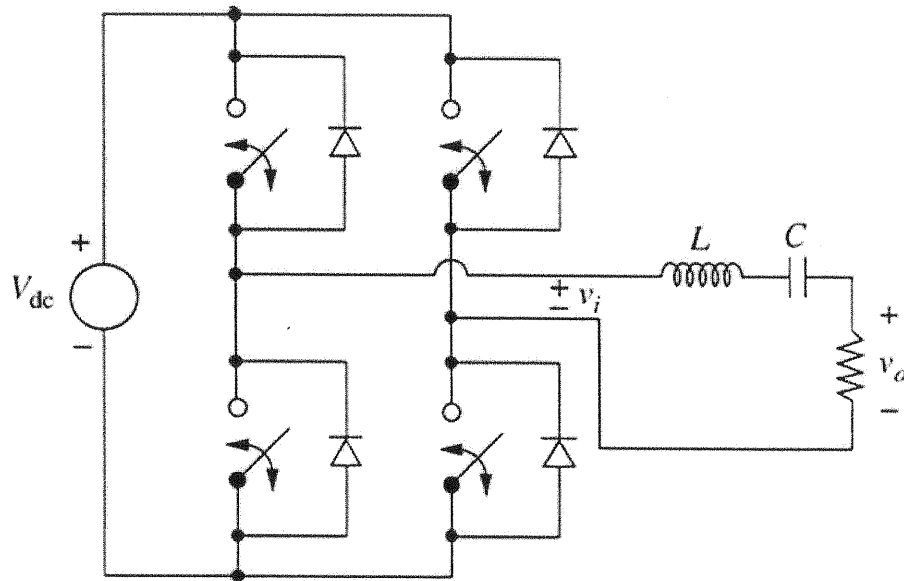


Figure 6

[10 marks]

(CLO3, CLO 5)

- b. The circuit illustrated in **Figure 7** shows an inverter circuit which converts a DC Power into AC power at desired output voltage and frequency. Switch pair in each leg, i.e. S1 S4, S3 S6 and S5 S2 are turned-on with a time interval of 180° . It means that switches S1 conducts for 180° and switch S4 for the next 180° of a cycle. This six-step three-phase inverter has an adjustable dc input. The load is a balanced Y connection with a series RL combination in each phase, with $R = 5\Omega$ and $L = 50 \text{ mH}$. The output frequency is to be varied between 30 and 60 Hz. **Determine the range of the dc input voltage required to maintain the fundamental-frequency component of current at 10 A rms.**

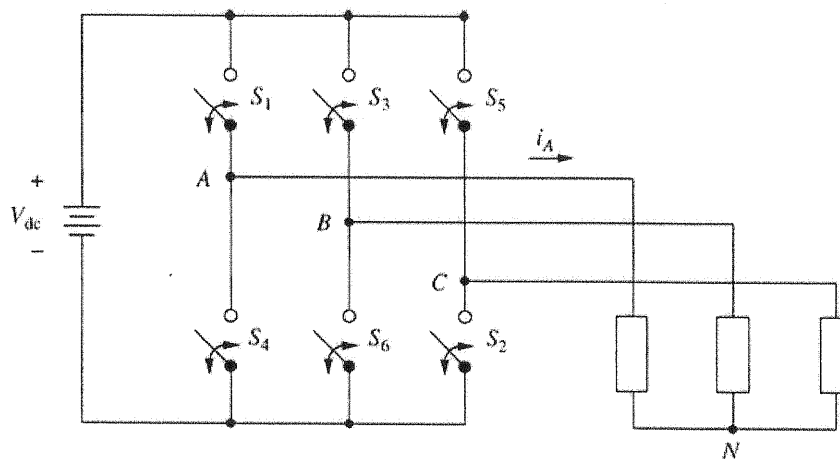


Figure 7

[10 marks]

(CLO 4)

END OF QUESTION

FORMULA'S

HALF-WAVE RECTIFIER

$$V_O = \frac{V_m}{\pi}$$

$$I_O = \frac{V_O}{R} = \frac{V_m}{\pi R}$$

$$V_{RMS} = \frac{V_m}{2}$$

$$I_{RMS} = \frac{V_m}{2R}$$

$$V_o = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$V_{o(RMS)} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

FULL-WAVE RECTIFIER

$$V_O = \frac{2V_m}{\pi}$$

$$I_O = \frac{V_O}{R} = \frac{2V_m}{\pi R}$$

$$V_O = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_O = \frac{V_O}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$

BUCK AND BOOST CONVERTER

$$I_L = \frac{V_s}{(1-D)^2 R}$$

$$I_L = \frac{V_{out}}{R}$$

$$\frac{\Delta V_O}{V_O} = \frac{D}{RCF}$$

$$\frac{\Delta V_O}{V_O} = \frac{1-D}{8LCf^2}$$

$$I_D = I_O = \frac{V_O}{R}$$

$$I_{L(max)} = I_L + \frac{\Delta i_L}{2}$$

$$I_{L(min)} = I_L - \frac{\Delta i_L}{2}$$


RESONANT INVERTER

$$\frac{V_o}{V_i} = \frac{R}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega L}{R} - \frac{1}{\omega RC}\right)^2}}$$


$$\omega_o = \frac{1}{\sqrt{LC}} \quad V_1 = \frac{4V_{dc}}{\pi}$$

$$Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC}$$

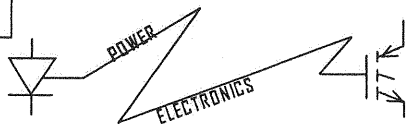
$$\frac{V_o}{V_i} = \frac{1}{\sqrt{1 + Q^2 \left(\frac{\omega}{\omega_o} - \frac{\omega_o}{\omega}\right)^2}}$$




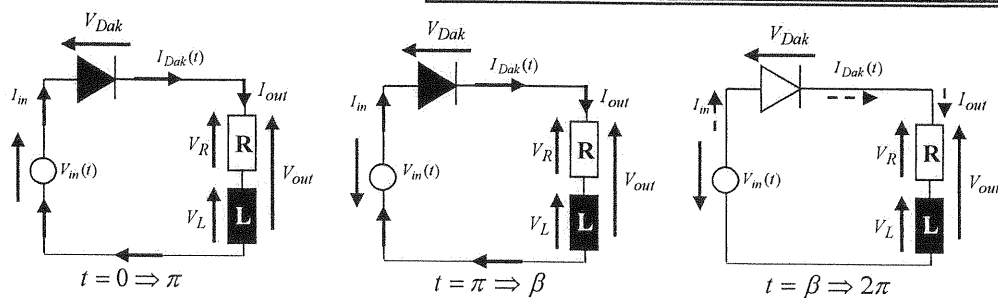POWER ELECTRONICS
WAVEFORM ANALYSIS
POWER CONVERTERS
H-W RECTIFICATION : R + L template



β
230°

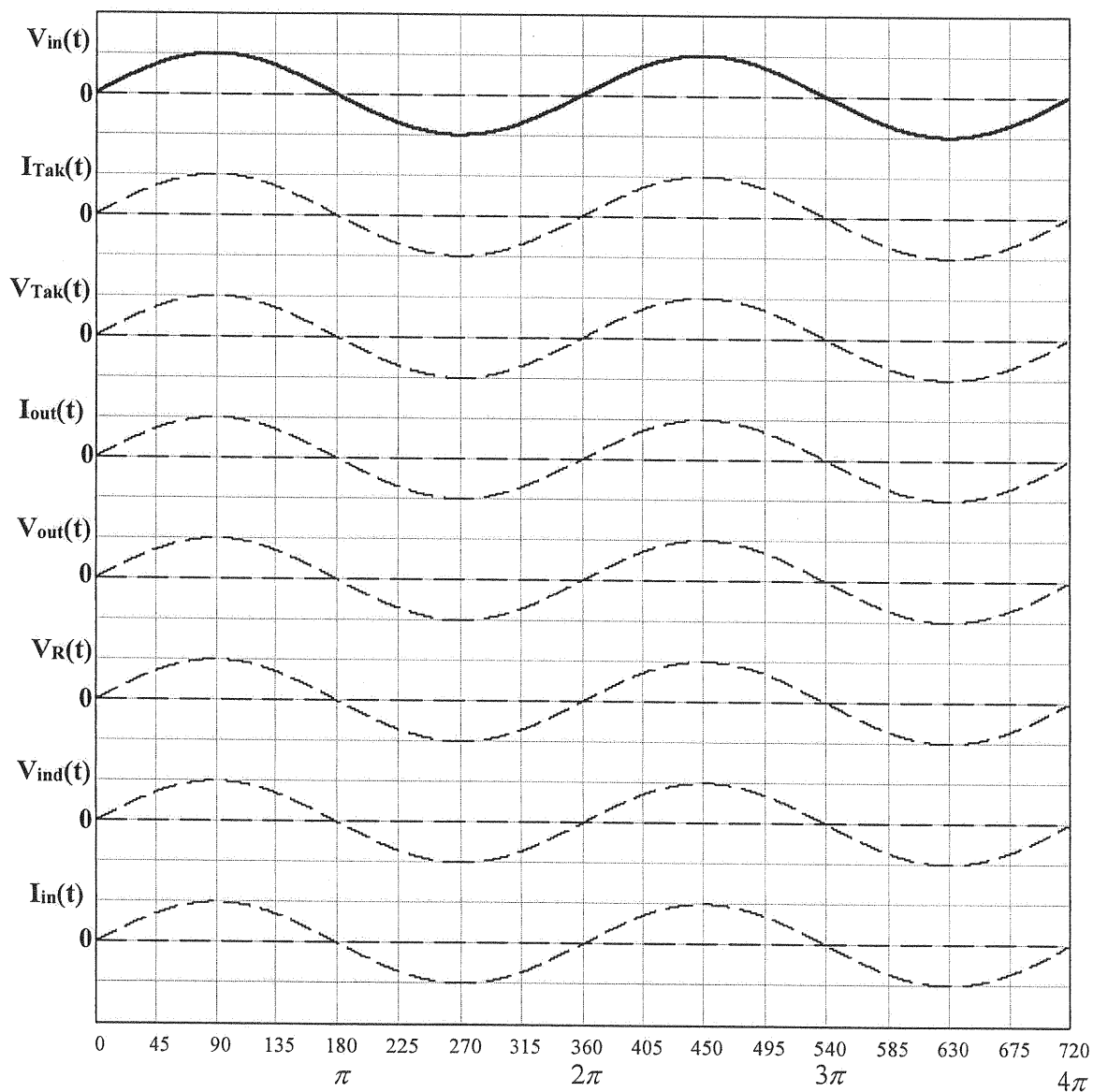

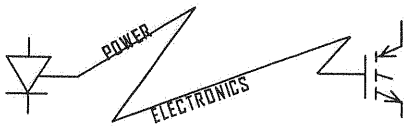


POWER ELECTRONICS

WAVEFORM ANALYSIS: PERFORMANCE CURVE

POWER CONVERTERS

FC-FW CONTROLLED RECTIFICATION : R

$I_{o(av)}$	SCALING FACTOR	I_{OAN}	versus	FIRING DELAY ANGLE α
$I_{o(rms)}$	SCALING FACTOR	I_{ORN}	versus	FIRING DELAY ANGLE α
$I_{o(M)}$	SCALING FACTOR	I_{OMN}	versus	FIRING DELAY ANGLE α
$I_{scr(av)}$	SCALING FACTOR	I_{AN}	versus	FIRING DELAY ANGLE α
$I_{scr(rms)}$	SCALING FACTOR	I_{RN}	versus	FIRING DELAY ANGLE α
CURRENT FORM FACTOR	ff_i		versus	FIRING DELAY ANGLE α

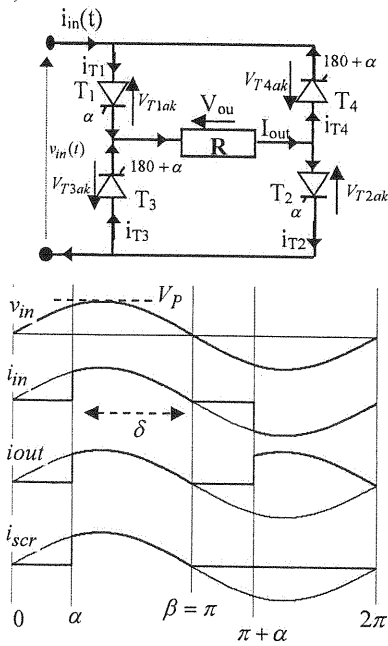

$$I_{out,av} = I_{OAN} \times \frac{V_P}{R}$$

$$I_{out,rms} = I_{ORN} \times \frac{V_P}{R}$$

$$I_{out,max} = I_{OMN} \times \frac{V_P}{R} = I_{in,max} = I_{scr,max}$$


$$I_{scr,av} = I_{AN} \times \frac{V_P}{R}$$




$$I_{scr,rms} = I_{RN} \times \frac{V_P}{R}$$

$$I_{OAN} = \frac{1 + \cos \alpha}{\pi} \Rightarrow \frac{2}{\pi} @ \alpha = 0$$

$$I_{ORN} = \sqrt{\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{2\pi}} \Rightarrow \frac{1}{\sqrt{2}} @ \alpha = 0$$
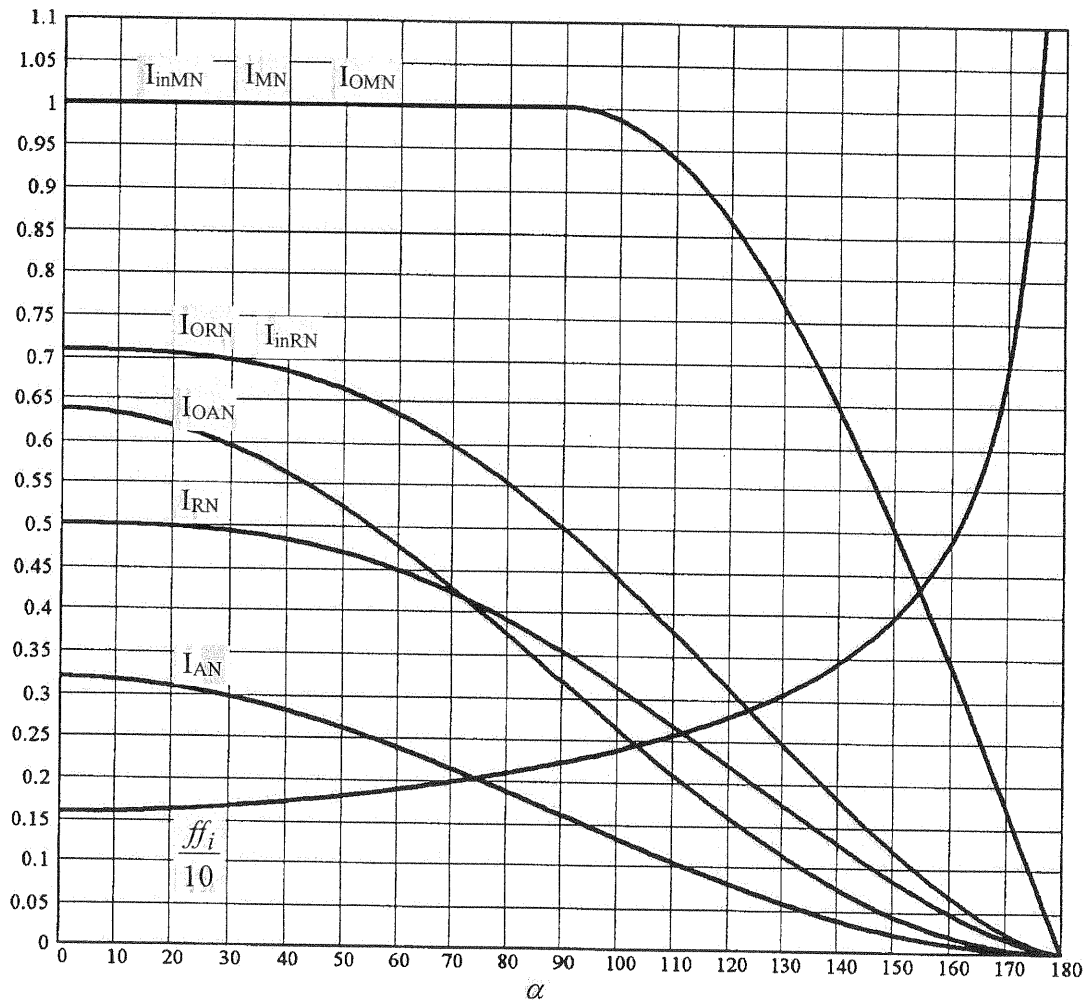
$$I_{OMN} = \sin \alpha @ \alpha \geq \frac{\pi}{2} \text{ or } 1 @ \alpha \leq \frac{\pi}{2}$$



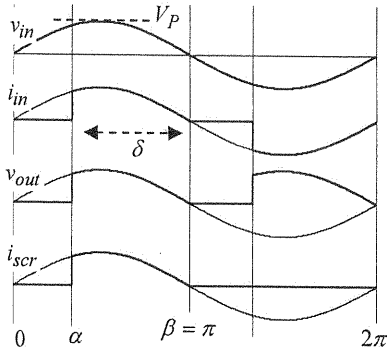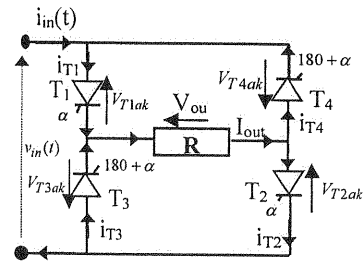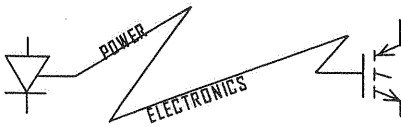

$$\begin{aligned}
 V_{out,av} &= V_{OAN} \times V_P \\
 V_{out,rms} &= V_{ORN} \times V_P \\
 V_{out,max} &= V_{OMN} \times V_P \\
 P_O &= P_{ON} \times P_M \\
 P_M &= V_{in,rms} \times I_{in,rms}(\alpha=0)
 \end{aligned}$$


$$V_{OAN} = \frac{1 + \cos \alpha}{\pi} \Rightarrow \frac{2}{\pi} @ \alpha = 0$$


$$V_{ORN} = \sqrt{\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{2\pi}} \Rightarrow \frac{1}{\sqrt{2}} @ \alpha = 0$$

$$V_{OMN} = \sin \alpha @ \alpha \geq \frac{\pi}{2} \text{ or } 1 @ \alpha \leq \frac{\pi}{2}$$

$$P_{ON} = \frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{\pi} \Rightarrow 1 @ \alpha = 0$$
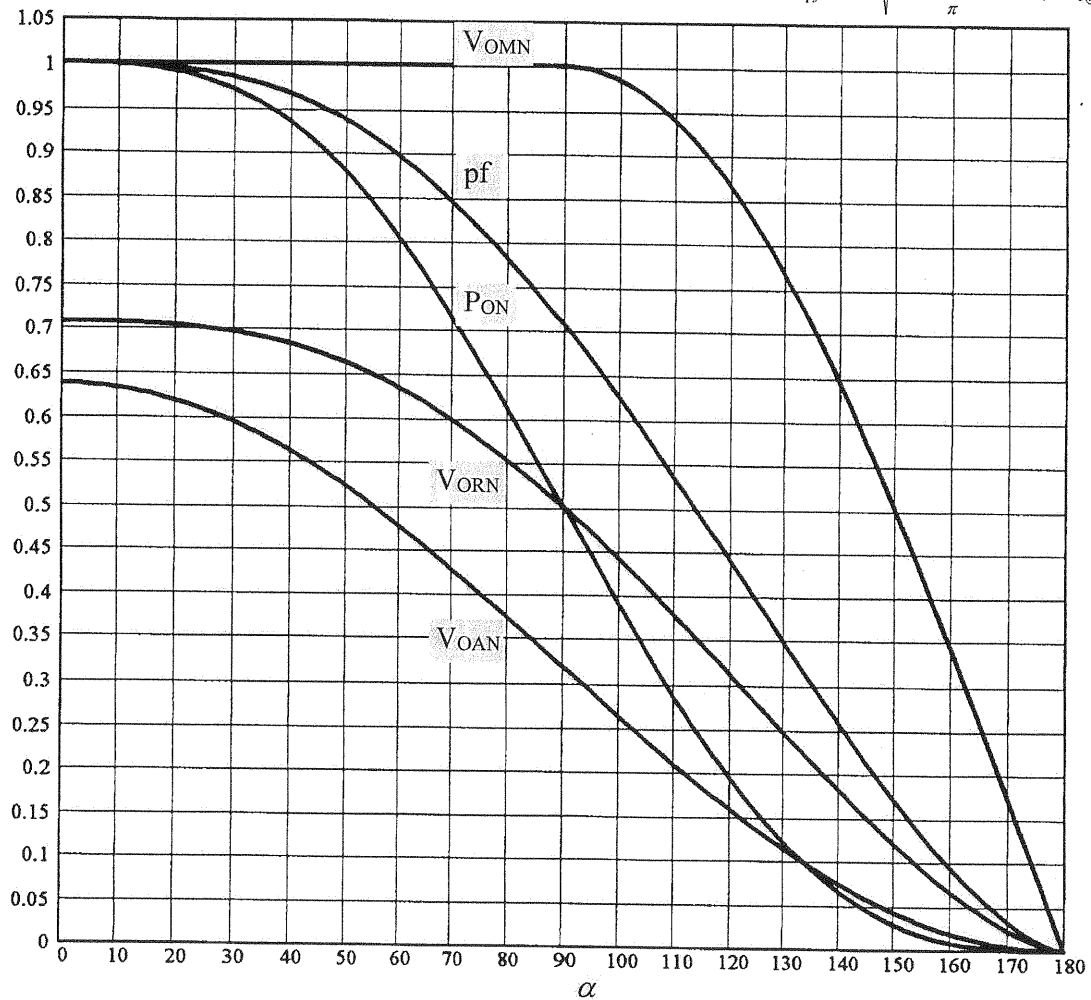
$$pf = \sqrt{\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{\pi}} \Rightarrow 1 @ \alpha = 0$$



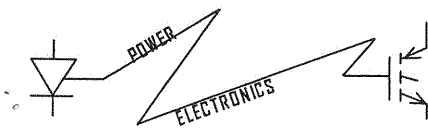

POWER ELECTRONICS

WAVEFORM ANALYSIS: PERFORMANCE CURVE

POWER CONVERTERS

FC-FW CONTROLLED RECTIFICATION : R



LINE CURRENT HARMONICS *versus* α

$I_{in(rms)}$ SCALING FACTOR I_{IRN} *versus* FIRING DELAY ANGLE α

$I_{infund(rms)}$ SCALING FACTOR I_{IFRN} *versus* FIRING DELAY ANGLE α

$I_{inharm(rms)}$ SCALING FACTOR I_{IHRN} *versus* FIRING DELAY ANGLE α

FUNDAMENTAL 3rd 5th 7th 9th HARMONICS

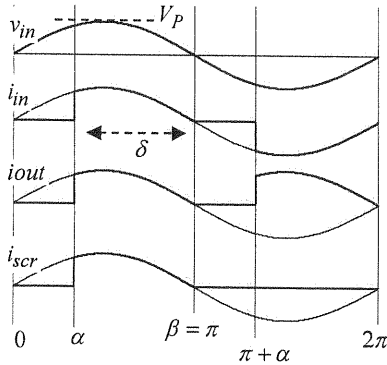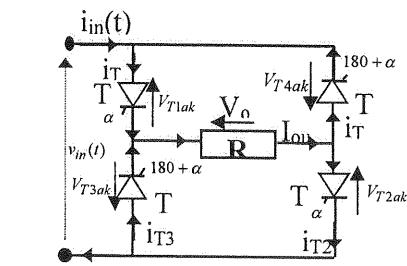

$$I_{IRN} = \sqrt{\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{\pi}}$$

$$I_{IFRN} = \sqrt{\left[1 - \frac{\alpha}{\pi} + \frac{\sin 2\alpha}{2\pi}\right]^2 + \left[\frac{\cos 2\alpha - 1}{4\pi}\right]^2}$$


$$I_{IHRN} = \sqrt{\frac{1}{\pi^2} \left\{ \left[\frac{\sin(n+1)\alpha}{n+1} \right] - \left[\frac{\sin(n-1)\alpha}{n-1} \right] \right\}^2 + \frac{1}{\pi^2} \left\{ \left[\frac{1 - \cos(n-1)\alpha}{n-1} \right] - \left[\frac{1 - \cos(n+1)\alpha}{n+1} \right] \right\}^2}$$

$$pf = \sqrt{\frac{\pi - \alpha + \frac{1}{2} \sin 2\alpha}{\pi}}$$

$$I_{in,rms} = I_{IRN} \times \frac{V_{in,rms}}{R}$$

$$I_{infund,rms} = I_{IFRN} \times \frac{V_{in,rms}}{R}$$
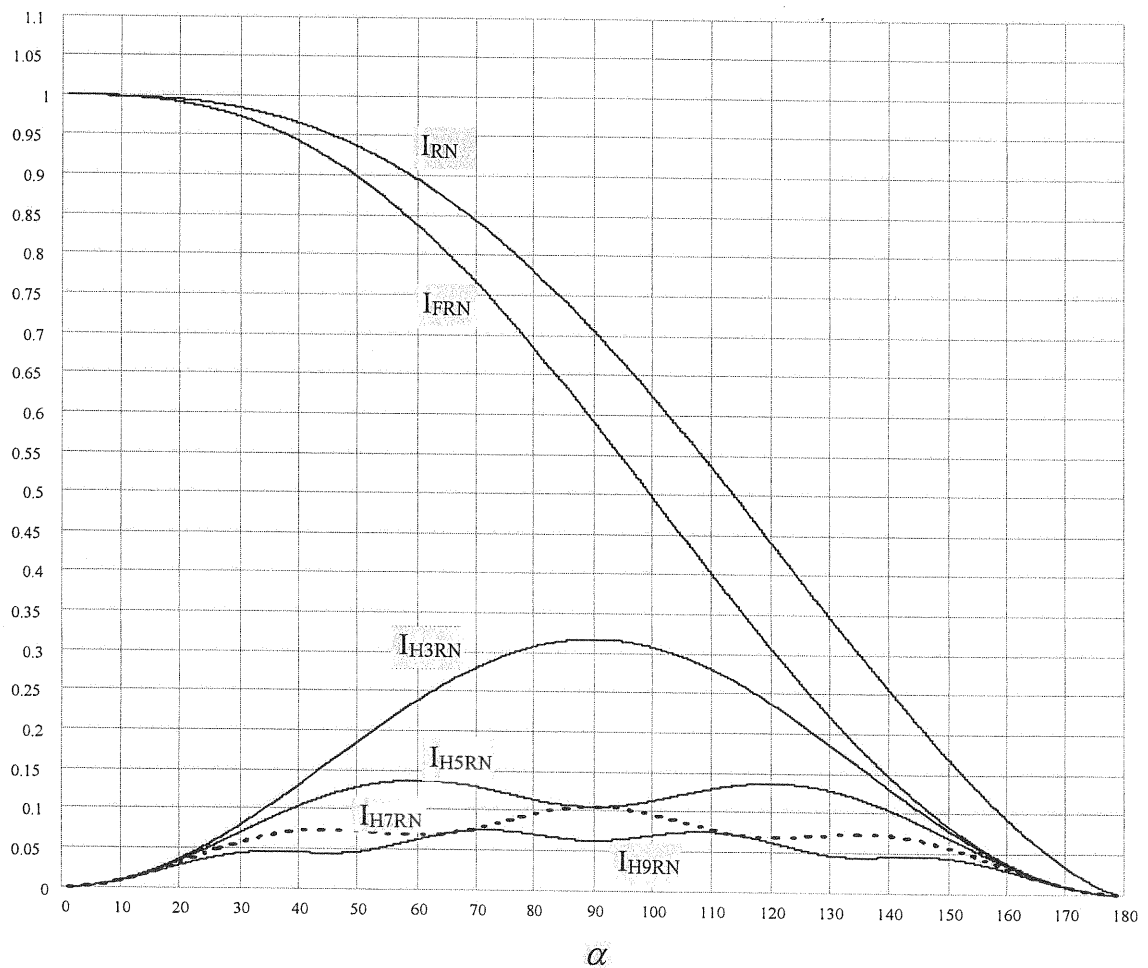
$$I_{inharm,rms} = I_{IHRN} \times \frac{V_{in,rms}}{R}$$



FORMULA'S

HALF-WAVE RECTIFIER

$$V_O = \frac{V_m}{\pi}$$

$$I_O = \frac{V_O}{R} = \frac{V_m}{\pi R}$$

$$V_{RMS} = \frac{V_m}{2}$$

$$I_{RMS} = \frac{V_m}{2R}$$

$$V_o = \frac{V_m}{2\pi} [1 + \cos \alpha]$$

$$V_{o(RMS)} = \frac{V_m}{2} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

BUCK AND BOOST CONVERTER

$$I_L = \frac{V_s}{(1-D)^2 R}$$

$$\frac{\Delta_O}{V_O} = \frac{D}{RCF}$$

$$I_D = I_O = \frac{V_O}{R}$$

$$I_{L(max)} = I_L + \frac{\Delta i_L}{2}$$

$$I_{L(min)} = I_L - \frac{\Delta i_L}{2}$$

$$V_o = V_s x D$$

FULL-WAVE RECTIFIER

$$V_O = \frac{2V_m}{\pi}$$

$$I_O = \frac{V_O}{R} = \frac{2V_M}{\pi R}$$

$$V_O = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_O = \frac{V_O}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$