



**UNIVERSITI KUALA LUMPUR
Malaysia France Institute**

**FINAL EXAMINATION
SEPTEMBER 2013 SESSION**

SUBJECT CODE : FLD 30103
SUBJECT TITLE : POWER ELECTRONIC AND DRIVES
LEVEL : DIPLOMA
TIME / DURATION : 2.5 HOURS
DATE :

INSTRUCTIONS TO CANDIDATES

1. Please read the instructions given in the question paper CAREFULLY.
 2. This question paper is printed on both sides of the paper.
 3. Please write your answers on the answer booklet provided.
 4. Answer should be written in blue or black ink except for sketching, graphic and illustration.
 5. This question paper consists of TWO (2) sections. Section A and B. Answer all questions in Section A. For Section B, answer two (2) question only.
 6. Answer all questions in English.
 7. Formula is appended.
-

THERE ARE 4 PAGES OF QUESTIONS, EXCLUDING THIS PAGE AND APPENDIX.

SECTION A (Total: 60 marks)**INSTRUCTION: Answer ALL questions.****Please use the answer booklet provided.****Question 1**

- (a) **List four** types of power electronics conversion in energy power converter.
(4 marks)
- (b) **Draw** single-phase bridge rectifier with resistive load circuits and explain the operation.
(6 marks)
- (c) **Explain** briefly the difference conversion of static applications and drive applications in power electronic system and **state two** examples each of them.
(10 marks)

Question 2

- (a) **Draw** a single-phase inverter with resistive load, **sketch** the output voltage and **explain** the operation.
(10 marks)
- (b) Prove that the DC output voltage (V_{DC}) of a single phase half-wave uncontrolled rectifier with resistive load is $V_{DC} = \frac{V_m}{\pi}$.

$$V_{DC} = \frac{1}{T} \int_0^{T/2} V_m \sin(\omega t) dt$$

(10 marks)

Question 3

- (a) Name and draw three types of DC to DC power converter.

(6 marks)

- (b) Name the type of converter in **Figure 1** and explain the operation when S is on and off.

(6 marks)

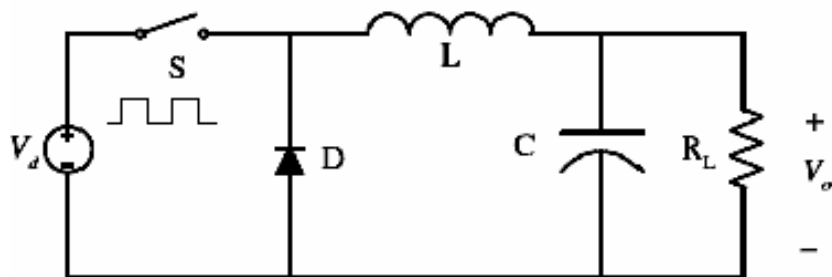


Figure 1

- (c) (i) Explain the concepts of unidirectional and bidirectional controllers for AC voltage controllers.

(4 marks)

- (ii) Explain the principles of On-Off Control for AC voltage controller in **Figure 2** and sketch the output voltage.

(4 marks)

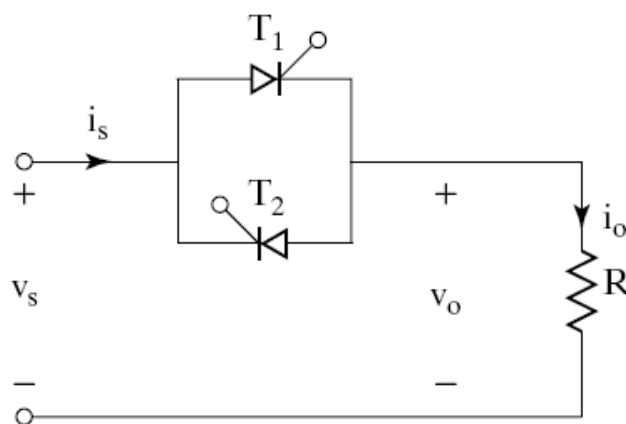
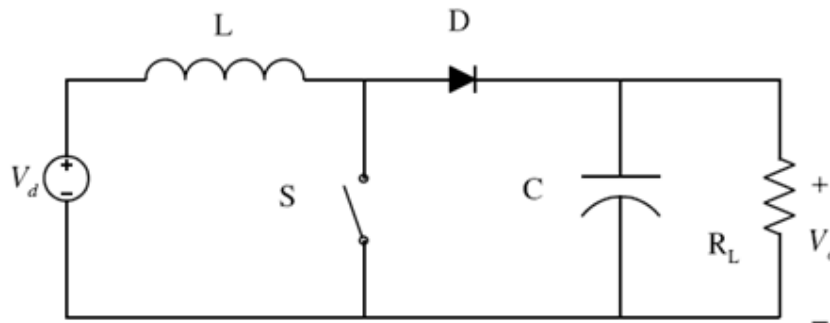


Figure 2

SECTION B (Total: 40 marks)**INSTRUCTION: Answer TWO (2) questions only****Please use the answer booklet provided.****Question 4**

- (a) **Figure 3** is the boost converter which has parameter supply voltage (V_s) = 24 V, duty cycle (D) = 0.7, load resistance (R_L) = 10 Ω , inductor (L) = 14 μH , capacitor (C) = 60 μF and the switching frequency is 200KHz. Determine,
- The output voltage V_o
 - the average, maximum and minimum inductor current (I_L , $I_{\max}$ and $I_{\min}$)
 - the output voltage ripples ($\frac{\Delta V_o}{V_o}$)
 - the average output current I_o

**Figure 3****(20 marks)****Question 5**

A single-phase half-wave controlled rectifier is connected to 120Vrms, 50 Hz source. The output of the rectifier is connected to a 10 ohm resistive load. If the average output voltage is 80% of the maximum possible output voltage, determine:

- the delay angle α
- the rms and average output voltage
- the average and rms thyristor current
- the input power factor

(20 marks)

Question 6

The AC voltage controller in **Figure 4** is connected to a resistive load $R = 30 \, \Omega$ and the input supply voltage $V_s = 240 \, \text{V}$ (rms), 50 Hz. The delay angles of thyristor T_1 and T_2 are equal: $\alpha_1 = \alpha_2 = 90^\circ$. Calculate

- (i) the rms output voltage
- (ii) the input power factor (PF)
- (iii) the average and rms thyristor current (I_A and I_R)

(20 marks)

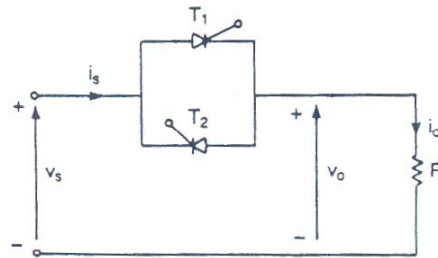


Figure 4

END OF QUESTION PAPER

APPENDIX

Performance Parameters of Rectifiers Formula

1. $P_{DC} = I_{DC} V_{DC}$
2. $P_{AC} = I_{RMS} V_{RMS}$
3. $\eta = \frac{P_{DC}}{P_{AC}}$
4. $V_{AC} = \sqrt{V_{RMS}^2 - V_{DC}^2}$
5. $FF = \frac{V_{RMS}}{V_{DC}}$
6. $RF = \frac{V_{AC}}{V_{DC}}$
7. $TUF = \frac{P_{DC}}{I_S V_S}$
8. $DF = \cos \phi$
9. $HF = \left(\frac{I_S^2 - I_{S1}^2}{I_{S1}^2} \right)^{\frac{1}{2}}$
10. $CF = \frac{I_{S(PEAK)}}{I_S}$
11. $PF = \frac{P_{REAL}}{P_{RMS}} = \frac{P_0}{VI} = \cos \phi$

Trigonometro Function

$$\int \sin nx dx = -\frac{\cos nx}{n}$$

Single phase half-wave controlled rectifier:

$$V_n = \frac{V_{dc}}{V_{dm}} = 0.5(1 + \cos \alpha), \quad V_m = \sqrt{2} \times V_s, \quad V_{dc} = \frac{V_m}{2\pi}(1 + \cos \alpha)$$

$$V_{rms} = \frac{V_m}{2} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}, \quad P_f = P_o / V_A$$

Single phase full-wave controlled rectifier:

$$V_n = \frac{V_{dc}}{V_{dm}}, \quad V_m = \sqrt{2} * V_s, \quad V_{dc} = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$V_{rms} = V_m \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}, \quad P_f = P_o / S \quad \text{where, } S = V_{rms} \times I_{rms}$$

Boost converter

$$V_o = V_s / (1 - D), \quad I_L = \frac{V_s}{(1 - D)^2 R}, \quad I_{max} = \frac{V_s}{(1 - D)^2 R} + \frac{V_s DT}{2L}, \quad I_{min} = \frac{V_s}{(1 - D)^2 R} - \frac{V_s DT}{2L}$$

$$I_o = V_o / R, \quad \frac{\Delta V_o}{V_o} = \frac{1 - D}{8LCf^2}$$

AC voltage controller

$$V_o = V_s \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}, \quad P_o = V_s I_o, \quad I_A = \frac{\sqrt{2} V_s}{2\pi R} (\cos \alpha + 1)$$

$$I_R = \frac{V_s}{\sqrt{2} R} \left[\frac{1}{\pi} \left(\pi - \alpha + \frac{\sin 2\alpha}{2} \right) \right]^{1/2}$$