



**UNIVERSITI KUALA LUMPUR
Malaysia France Institute**

**FINAL EXAMINATION
JANUARY 2014 SESSION**

SUBJECT CODE : NMB 20102
SUBJECT TITLE : ELECTRONICS ENGINEERING
LEVEL : BACHELOR
TIME / DURATION : 2.5 HOURS
DATE :

INSTRUCTIONS TO CANDIDATES

- 1. Please read the instructions given in the question paper CAREFULLY.**
 - 2. This question paper is printed on both sides of the paper.**
 - 3. Please write your answers on the answer booklet provided.**
 - 4. Answer should be written in blue or black ink except for sketching, graphic and illustration.**
 - 5. This question paper consists of TWO (2) sections. Section A and B. Answer all questions in Section A. For Section B, answer TWO (2) question only.**
 - 6. Answer all questions in English.**
 - 7. Do not open the question paper until instructed to do so.**
-

THERE ARE 8 PAGES OF QUESTIONS AND 1 PAGE OF APPENDIX, EXCLUDING THIS PAGE.

SECTION A (Total: 40 marks)**INSTRUCTION: Answer ALL questions.****Please use the answer booklet provided.****Question 1**


The electrical behavior of diode can be described with ideal and practical models. Draw both models.

(4 marks)

Question 2

The circuit shown on **Figure 1** is a zener diode voltage regulator. If $V_S = 10\text{ V}$, $R_2 = 100\ \Omega$, $V_Z = 6\text{ V}$, $I_{ZK} = 1\text{ mA}$, find the minimum value of R_1 so that the zener diode stays in the breakdown region.

(10 marks)

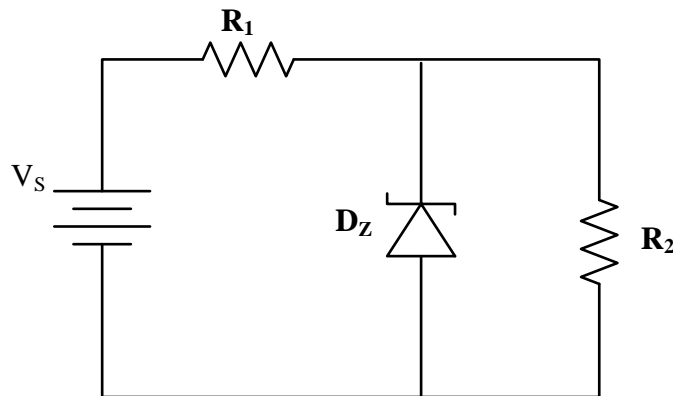**Figure 1**

Question 3

Determine the beta rating for the BJT shown in **Figure 2**. Then determine the value of I_C using both the alpha rating and the beta rating of the BJT.

(6 marks)

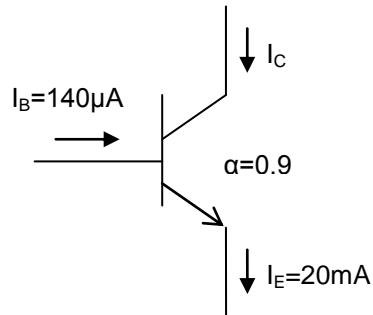


Figure 2

Question 4

(a) Convert the following binary numbers to decimal.

(i) 10010001

(4 marks)

(ii) 10111101.011

(6 marks)

(b) Draw the logic circuit that implements the expression

$$x = \bar{A}.B.C(\bar{A} + D)$$

(10 marks)

SECTION B (Total: 60 marks)

INSTRUCTION: Answer only TWO (2) questions.

Please use the answer booklet provided.

Question 5

- (a) Suppose the zener diode in **Figure 3** has a breakdown voltage of 10 V. Calculate the minimum and maximum zener currents. (8 marks)



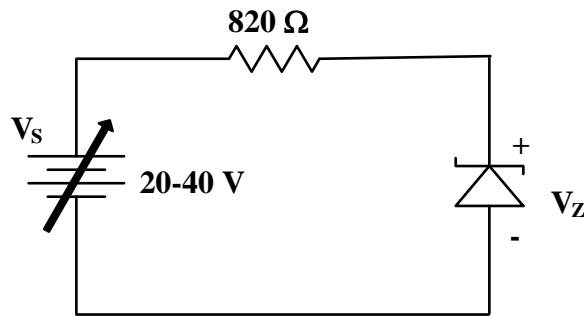


Figure 3

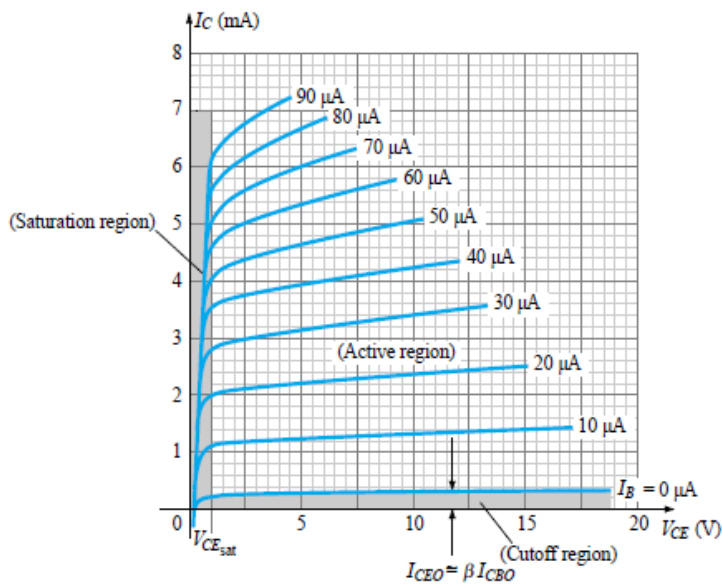- (b) Using the characteristics in **Figure 4**, determine:
- (i.) The value of I_C corresponding to $V_{BE} = +0.75\text{ V}$ and $V_{CE} = +5\text{ V}$. (4 marks)
 - (ii.) The value of V_{CE} and V_{BE} corresponding to $I_C = 3\text{ mA}$ and $I_B = 30\text{ }\mu\text{A}$. (6 marks)



(a)

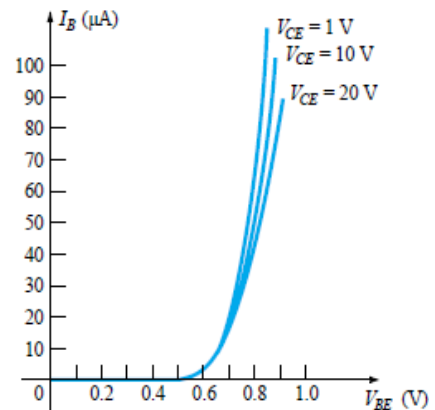

(b)

Figure 4

(c) Answer the following questions:

(i) Convert the following decimal numbers (58, 125 and 19) into the binary numbering system.

(6 marks)

(ii) Digital circuit in **Figure 5** shows the combinational logic circuit with three inputs and one output. Give the Boolean algebra for **S**, **X** and **Y**.

(6 marks)

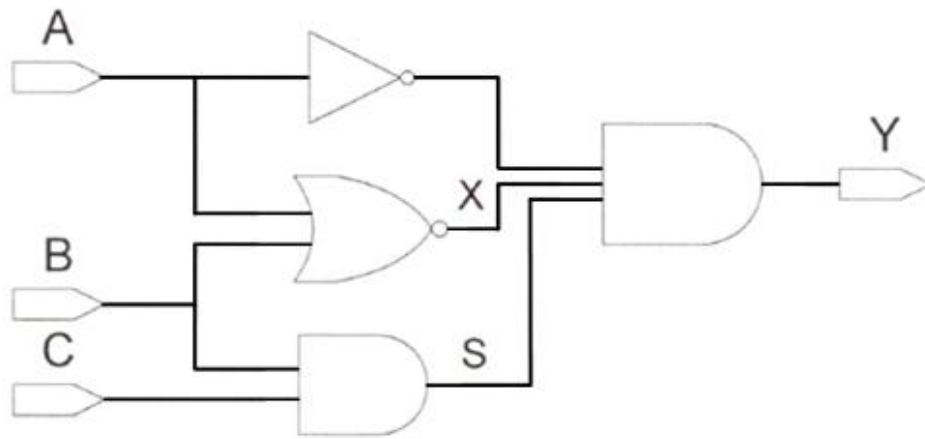


Figure 5

Question 6

- (a) The zener diode circuit in **Figure 6** has zener voltage of 9 V. Given that $V_S = 27\text{ V}$, $R_S = 15\text{ k}\Omega$, and $R_L = 10\text{ k}\Omega$. Assuming that the zener diode is operating in the breakdown region, calculate the current I_S , I_L , and I_Z shown in the circuit.

(6 marks)

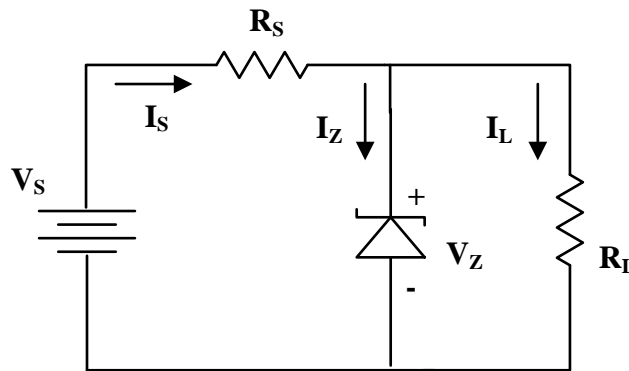


Figure 9

- (b) A water height sensor module in **Figure 7** uses a silicon based bipolar junction transistor to energize and operate a $12V_{DC}$ relay. The operation of the circuit is as follows: When sensor detects water, switch is closed and the BJT shall turn 'ON'. The relay then will be energized. Given $\beta = 100$, determine I_B , I_C , I_E , V_{BE} , V_{CE} and V_{CB} .

(12 marks)

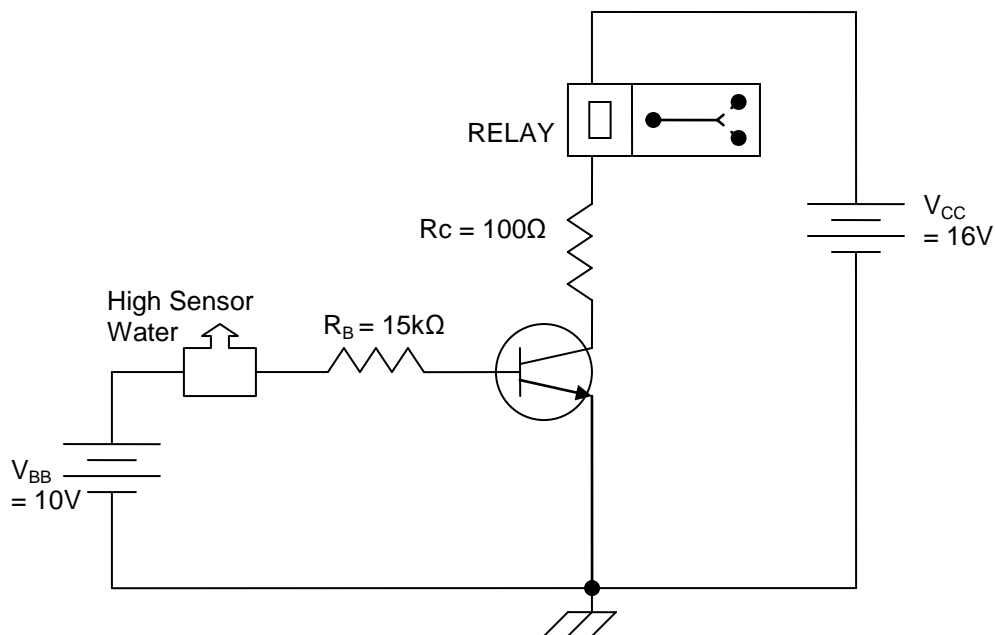


Figure 7

(c) Answer the following questions:

(i) Determine the binary numbers for the following hexadecimal numbers:

- $10A4_{16}$
- $CF8E_{16}$

(6 marks)

(ii) Design the logic circuit that has three inputs A, B and C, and whose output will be HIGH only when a majority of the inputs are HIGH. The design should include the truth table and Boolean expression and circuit diagram.

(6 marks)

Question 7

- (a) Consider the half wave rectifier circuit in **Figure 8**.
- (i) Draw the resultant output voltage for the circuit. (3 marks)
- (ii) Derive the expression for DC voltage output if $V_1 = V_M \cdot \sin \theta$ where V_M is the peak voltage and θ is the electrical angle. (5 marks)

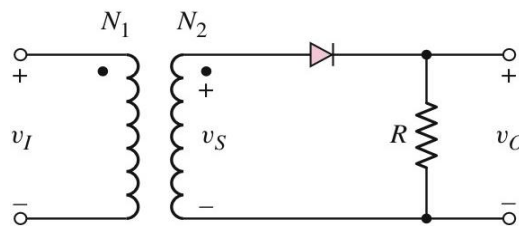


Figure 8

- (b) (i) Given the information in **Figure 9**, determine I_C , V_{CC} , β , and R_B . Consider germanium based BJT. (8 marks)
- (ii) Find the saturation current I_{Csat} for the same circuit configuration. (4 marks)

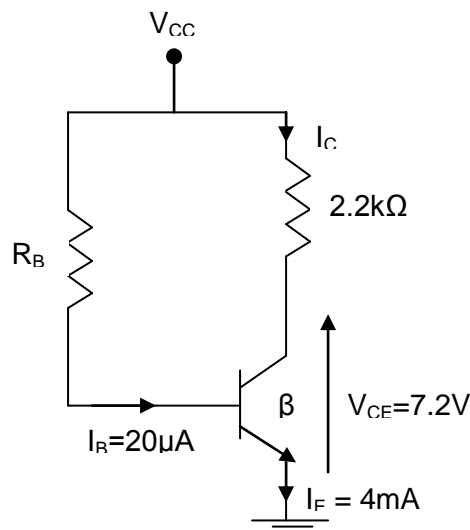


Figure 9

(c) Answer the following questions:

(i) Convert the following hexadecimal number to binary:

- 38_{16}
- 59_{16}
- $A14_{16}$
- $5C8_{16}$

(4 marks)

(ii) Simplify the circuit diagram in **Figure 10** using demorgan theorem or boolean equation.

(6 marks)

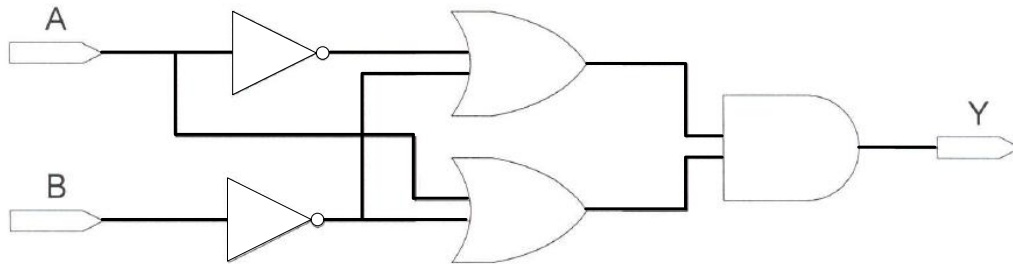


Figure 10

END OF QUESTION PAPER

APPENDIX 1

BOOLEAN THEOREMS

- | | | |
|---------------------------------|---|--|
| 1. $X \bullet 0 = 0$ | 8. $X + \overline{X} = 1$ | 14. $X + XY = X$ |
| 2. $X \bullet 1 = X$ | 9. $X + Y = Y + X$ | 15. $X + \overline{X}Y = X + Y$ |
| 3. $X \bullet X = X$ | 10. $X \bullet Y = Y \bullet X$ | 16. $\overline{X + Y} = \overline{X} \overline{Y}$ |
| 4. $X \bullet \overline{X} = 0$ | 11. $X + (Y + Z) = (X + Y) + Z = X + Y + Z$ | 17. $\overline{XY} = \overline{X} + \overline{Y}$ |
| 5. $X + 0 = X$ | 12. $X(YZ) = (XY)Z = XYZ$ | 18. $\overline{\overline{A}} = A$ |
| 6. $X + 1 = 1$ | 13a. $X(Y + Z) = XY + XZ$ | |
| 7. $X + X = X$ | 13b. $(W + X)(Y + Z) = WY + XY + WZ + XZ$ | |