



**UNIVERSITI KUALA LUMPUR
Malaysia France Institute**

**FINAL EXAMINATION
SEPTEMBER 2014 SESSION**

SUBJECT CODE : FLD20403
SUBJECT TITLE : DIGITAL SYSTEM
LEVEL : DIPLOMA
**TIME / DURATION : 2.00 PM – 5.00 PM
(3 HOURS)**
DATE : 30 DECEMBER 2014

INSTRUCTIONS TO CANDIDATES

1. Please read the instructions given in the question paper **CAREFULLY**.
 2. This question paper is printed on both sides of the paper.
 3. Please write your answers on the answer booklet provided.
 4. Answers should be written in blue or black ink except for sketching, graphic and illustration.
 5. This question paper consists of **TWO (2)** sections. Section A and B. Answer all questions in Section A. For Section B, answer two (2) questions only.
 6. Answer all questions in **English**.
-

THERE ARE 4 PAGES OF QUESTIONS, EXCLUDING THIS PAGE AND APPENDIX.

SECTION A (Total: 60 marks)**INSTRUCTION: Answer ALL questions.****Please use the answer booklet provided.****Question 1**

- (a) Convert 1011011101_2 to hexadecimal and decimal (4 marks)
- (b) Convert the octal number $(36.065)_8$ to binary and hexadecimal (4 marks)
- (c) Perform the following operations by using an 8-bit, 2's
- i. $-29_{10} + (-43_{10})$ (4 marks)
- ii. $-66_{10} - (-75_{10})$ (4 marks)
- (d) The $110\ 0101_2 + 1110\ 1000_2$ is an 8-bit, 2's complement number.
Perform the operation. Convert the answer to decimals. (4 marks)
- (e) Add the following decimal numbers in BCD, and verify the answer in decimals
 $39_{10} + 69_{10}$ (4 marks)
- (f) Add the following Hexadecimal number. Show your work.
 $DA_{16} - 2E_{16}$ (2 marks)

Question 2

Simplify the following Boolean expressions using the De'Morgan theorems and/or Boolean algebra.

(a) $M = \bar{A}C + \bar{A}\bar{C}D + ABC + AB\bar{C}D$ (4 marks)

(b) $Q = \overline{AB + \bar{C}D + EF}$ (4 marks)

Question 3

Based on the logic circuit of Figure 1:

(a) Determine the Boolean expression for the output Y (4 marks)

(b) Simplify the expression determined in (a) using the De'Morgan theorems and/or Boolean algebra. (4 marks)

(c) Draw the simplified circuit of expression (b) (4 marks)

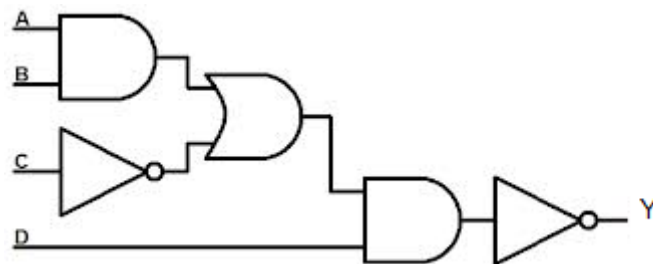


Figure 1

Question 4

Implement the following Boolean expression with a 4 x 1 multiplexer

$$J(A, B, C, D) = \sum_m (0, 1, 3, 4, 8, 9, 15)$$

(a) Tabulate the truth table (8 marks)

(b) Draw the circuit (6 marks)

SECTION B (Total: 40 marks)**INSTRUCTION: Answer only TWO (2) questions****Please use the answer booklet provided.****Question 5**

Implement the truth table of Table 1 given below using any basic logic gate and:

- (a) A single 3-to-8 Decoder and any simple logic gate (7 marks)
- (b) A single 8-to-1 Multiplexer and any simple logic gate (7 marks)
- (c) A single 4-to-1 Multiplexer and any simple logic gate (6 marks)

Table 1

Input			Output
a	b	c	Y
0	0	0	1
0	0	1	0
0	1	0	X
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	1

Question 6

- (a) Figure 2 shows a 3-bit synchronous counter using JK flip flop.
- i. Derive the input equations for each flip-flop. (3 marks)
 - ii. Determine the MOD number of the counter. (3 marks)
 - iii. Draw the state table and state diagram for the circuit (6 marks)

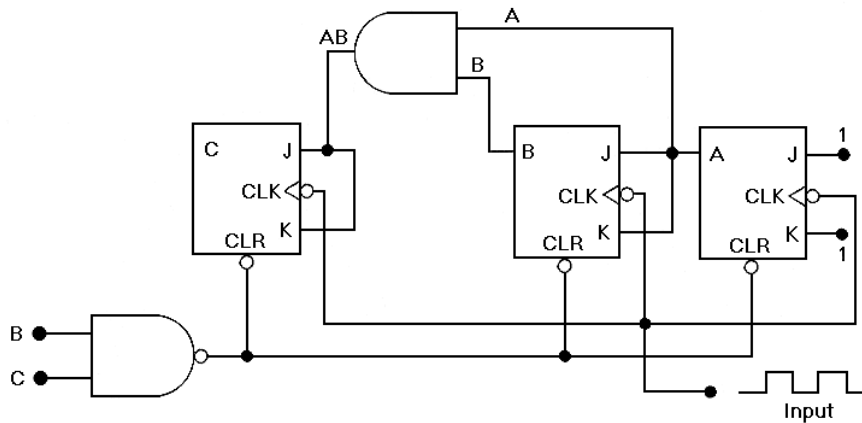


Figure 2

- (b) How many FFs are required for the MOD-60 counter? (2 marks)
- (c) Construct a MOD-10 counter that will count from 0000 through 1001 (6 marks)

Question 7

Design a combinational circuit that converts a 4-bit gray code to a 4-bit binary number.

- Tabulate its truth table (8 marks)
- Simplify the expression using K-map (7 marks)
- Implement the circuit using exclusive-OR gates (5 marks)

END OF QUESTION PAPER

APPENDIX

Boolean algebra and De Morgan's theorems

- | | | |
|---------------------------------|---|--|
| 1. $X \bullet 0 = 0$ | 8. $X + \overline{X} = 1$ | 14. $X + XY = X$ |
| 2. $X \bullet 1 = X$ | 9. $X + Y = Y + X$ | 15. $X + \overline{XY} = X + Y$ |
| 3. $X \bullet X = X$ | 10. $X \bullet Y = Y \bullet X$ | 16. $\overline{X + Y} = \overline{X} \overline{Y}$ |
| 4. $X \bullet \overline{X} = 0$ | 11. $X + (Y + Z) = (X + Y) + Z = X + Y + Z$ | 17. $\overline{XY} = \overline{X} + \overline{Y}$ |
| 5. $X + 0 = X$ | 12. $X(YZ) = (XY)Z = XYZ$ | 18. $\overline{\overline{A}} = A$ |
| 6. $X + 1 = 1$ | 13a. $X(Y + Z) = XY + XZ$ | |
| 7. $X + X = X$ | 13b. $(W + X)(Y + Z) = WY + XY + WZ + XZ$ | |