



UNIVERSITI KUALA LUMPUR
MALAYSIAN INSTITUTE OF MARINE ENGINEERING TECHNOLOGY

FINAL EXAMINATION
SEPTEMBER 2016 SEMESTER

COURSE CODE : LEB 10403
COURSE NAME : DIGITAL ELECTRONIC
PROGRAMME NAME : BACHELOR OF MARINE ELECTRICAL ELECTRONIC
(FOR MPU: PROGRAMME LEVEL)
DATE : 16TH JANUARY 2017
TIME : 2.00PM
DURATION : 3 HOURS

INSTRUCTIONS TO CANDIDATES

1. Please **CAREFULLY** read the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **TWO (2)** sections; Section A and Section B.
4. Answer **ALL** questions in Section A. For Section B, answer **THREE (3)** questions **WITH AT LEAST ONE (1)** question from question 4 or question 5.
5. Please write your answers on the answer booklet provided.
6. Answer all questions in English language **ONLY**.

THERE ARE 7 PAGES OF QUESTIONS, INCLUDING THIS PAGE.

SECTION A (Total: 40 marks)

INSTRUCTION: Answer ALL questions.
Please use the answer booklet provided.

Question 1

a) Convert the binary number below to their decimal equivalent. (*Course Learning Outcome 1*)

- i. 01101011₂
- ii. 10010101₂
- iii. 11011110₂

[6 marks]

b) Convert the decimal number below to their BCD equivalent. (*Course Learning Outcome 1*)

- i. 187₁₀
- ii. 962₁₀, and
- iii. 529₁₀

[6 marks]

c) Rewrite **Table Q1 (c)** below in you answer booklet. Fill in the table by indicating the 8 – bit sign – and – magnitude, 1’s complement and 2’s complement representation for each of the decimal number. (*Course Learning Outcome 1*)

Table Q1 (c)

Decimal	Sign – and – magnitude	1’s complement	2’s complement
+ 30			
+ 13			
- 6			
- 15			

[8 marks]

Question 2

- a. Simplify the following Boolean expressions using Boolean algebra.

(Course Learning Outcome 2)

i. $W = (\bar{A} + B)C + ABC$

[3 marks]

ii. $X = AB + (\bar{A} + \bar{B})C + AB$

[3 marks]

- b. Given the function $F(A,B,C) = (A + B)(C + \bar{B})$

(Course Learning Outcome 2)

- i. Convert the given function to a standard sum – of – product (SOP) form.

[4 marks]

- ii. Construct the truth table for the standard SOP form.

[4 marks]

- iii. Draw the Karnaugh Map and express the simplified equation, and

[3 marks]

- iv. Sketch the logic circuit of the simplified equation in (iii).

[3 marks]

SECTION B (Total: 60 marks)

INSTRUCTION: Answer THREE (3) ONLY from FOUR (4) questions.

Please use the answer booklet provided.

Question 3

a) Sketch the corresponding logic circuit diagram for the following expressions using ONLY AND gate, OR gate and INVERTER. (Course Learning Outcome 2 & 3)

i. $X = \overline{AB(C + \overline{D})}$

[4 marks]

ii. $Y = \overline{M + N} + (\overline{P}Q)$

[4 marks]

b) Derive and simplify the expression from the corresponding logic circuit diagram in Figure Q3 (b).

(Course Learning Outcome 2 & 3)

 


Figure Q3 (b)

[2 marks]

c) Derive and simplify the expression from the corresponding logic circuit diagram in Figure Q3 (c).

(Course Learning Outcome 2 & 3)

 


Figure Q3 (c)

[2 marks]

d) Draw the following expression **ONLY** by using **NAND gates**.
 (Course Learning Outcome 2 & 3)

- i. $X = ABC$
- ii. $Y = \overline{EF} + \overline{GH}$

[8 marks]

Question 4

a) Produce all outputs shown in Table: 1 into a standard Sum-of-Product (SOP) format. (Course Learning Outcome 3)

X	Y	Z	Q
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

Table: 1

[5 marks]

b) Given the function $F(A,B,C) = \overline{AC} + \overline{ABC} + \overline{AB} + \overline{AB} + \overline{ABC} + ABC$
 (Course Learning Outcome 4)

- i) Produce the truth table for the output, F
- ii) Use the Karnaugh Map and write the simplified Boolean expression
- iii) Draw the basic logic circuit for the simplified expression in part (b)(ii)
- iv) Express the output F , in sum-of-products (SOP) form, and
- v) Redraw the circuit in part (c) using NAND gates only.

[3 marks]

[3 marks]

[3 marks]

[3 marks]

[3 marks]

Question 5

- a) Digital bits transmission can be done in serial or parallel. Describe the main differences between synchronous and asynchronous counters. (*Course Learning Outcome 5*)

[4 marks]

- b) Design MOD 7 synchronous count up counter by using JK flip flop. Take the negative going transition clock (NGT) as the input. The design should include the following: (*Course Learning Outcome 5*)

- i. The state diagram of the counter

[4 marks]

- ii. The state transition table

[4 marks]

- iii. K-maps to simplify each JK signal, and

[4 marks]

- iv. Design the complete counter circuit.

[4 marks]

Question 6

- a) Design MOD 8 asynchronous count up counter by using JK flip flop. The design should include the followings: (*Course Learning Outcome 5*)

- i. The state transition diagram

[4 marks]

- ii. K-maps to simplify each JK signal

[4 marks]

- iii. Design the complete counter circuit

[4 marks]

b) Describe the main operation of 2-to-4 line decoder (active high) which has variable A and B as its input. Produce the followings: (*Course Learning Outcome 3*)

i. A complete truth table, and

[4 marks]

ii. Schematic diagram of the decoder.

[4 marks]

END OF QUESTIONS