



UNIVERSITI KUALA LUMPUR
KAMPUS CAWANGAN MALAYSIAN SPANISH INSTITUTE

FINAL EXAMINATION
JULY 2023 SEMESTER

COURSE CODE : SRD 11403
COURSE NAME : ELECTRICAL TECHNOLOGY
PROGRAMME NAME : DIPLOMA
DATE : 27 SEPTEMBER 2023
TIME : 9.00 AM – 11.00 AM
DURATION : 2 HOURS

INSTRUCTIONS TO CANDIDATES

1. Please **CAREFULLY** read the instructions given on the question paper. This question paper has information printed on both sides of the paper.
 2. This question paper consists of **TWO (2)** sections: Section A and Section B.
 3. Answer **ALL** questions from Section A in the OMR answer sheet provided.
 4. Answer **THREE (3)** questions **ONLY** from Section B in the answer booklet provided.
 5. Answer all questions in English language **ONLY**.
 6. Formula sheet is appended.
-

THERE ARE 10 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.

SECTION A (Total: 25 marks)

INSTRUCTION: Answer ALL questions.

1. Determine which portion of an atom has no electrical charge.
 - A. electron
 - B. proton
 - C. neutron
 - D. neutral

2. All the effects of electric current take place because of the movement of _____.
 - A. free electron
 - B. free proton
 - C. free neutron
 - D. nucleus

3. An atom having more electrons than protons is said to be _____.
 - A. positively charged
 - B. negatively charged
 - C. neutrally charged
 - D. discharged

4. Select the appropriate prefix for $150 \times 10^{-3} \text{ H}$.
 - A. 0.15H
 - B. 150kH
 - C. 150mH
 - D. 150 μ H

5. Which of the following metric prefixes could replace 10^{-12} ?
 - A. micro
 - B. mega
 - C. kilo
 - D. pico

6. Add 21 mA and 8000 μ A and express the result in milliamperes.
- A. 290 mA
 - B. 29 mA
 - C. 218 mA
 - D. 21.8 mA
7. The rate at which work is performed is called _____.
- A. current
 - B. energy
 - C. power
 - D. voltage
8. ***“The internal friction which retards the flow of current (electrons) through a material”.***
- The statement can best be described for _____.
- A. power
 - B. voltage
 - C. resistance
 - D. current
9. Ohm's law is a relationship between _____.
- A. voltage, current and time
 - B. current, power and resistance
 - C. resistance, time and current
 - D. voltage, current and resistance
10. In a series circuit, which of the parameters remain constant across all circuit elements such as resistor, capacitor, and inductor?
- A. Voltage
 - B. Current
 - C. Both above
 - D. None of the above

11. Convert the following capacitance value, 22nF to μF .
- A. 0.022 μF
 - B. 0.00055 μF
 - C. 0.22 μF
 - D. 200nF
12. A 10 V battery is connected across four 100 Ω resistors in series. What is the value of the current that flows through each resistor?
- A. 2.5 mA
 - B. 25 mA
 - C. 250 mA
 - D. 0.25 mA
13. Five equal values of resistors are connected in series with a 20V source. A current of 4mA is measured in the circuit. What could be the value for each resistor connected in the circuit?
- A. 1k Ω
 - B. 5k Ω
 - C. 125 Ω
 - D. 20 Ω
14. Which of the following electrical magnitude is the common reference for a parallel circuit?
- A. resistance
 - B. current
 - C. voltage
 - D. power
15. As additional resistors are connected to a parallel circuit, predict what will happen to the total resistance in the circuit.
- A. increase
 - B. increase by the value of the resistor being connected
 - C. decrease
 - D. remain unchanged

16. A 50Ω resistor is connected in parallel with another 15Ω resistor. What will be the value of total resistance in the circuit?
- A. 17.1Ω
 - B. 11.5Ω
 - C. 16.5Ω
 - D. 74Ω
17. The total current entering a junction may be different from the total current leaving the junction. Relate your understanding to the Kirchoff Current Law (KCL).
- A. True
 - B. False
18. The rate of changing direction is called the frequency of the AC. It is measured in hertz (Hz), which refers to the number of forwards-backwards cycles per second.
- A. True
 - B. False
19. Which of the following is not the magnitude of a sinusoidal wave in an AC system?
- A. Peak value
 - B. Root mean square value
 - C. Resistive value
 - D. None of the above
20. The opposition to alternating current by a capacitor is known as capacitive reactance.
- A. True
 - B. False
21. In a series RC network, the capacitive reactance tends to increase as frequency increases.
- A. True
 - B. False

22. As the supply frequency increases in a series RL network, the inductive reactance also increases.
- A. True
 - B. False
23. ***“The effective resistance of an electric circuit or component to alternating current, arising from the combined effects of ohmic resistance and reactance.”***
The above statement is best described by _____.
- A. Resistance
 - B. Inductance
 - C. Impedance
 - D. Reactance
24. In a series RLC network, the reactance of both capacitor and inductor tends to cancel each other.
- A. True
 - B. False
25. If the capacitive reactance (X_C) is less than the inductive reactance (X_L) in a series RLC network, the circuit is predominantly inductive. Which of the following best described the effect on voltage and current in the circuit?
- A. current leads voltage by θ°
 - B. current lags voltage by θ°
 - C. both voltage and current are in the same phase angle
 - D. none of the above

SECTION B (Total: 75 marks)

INSTRUCTION: Answer THREE (3) questions ONLY.

Question 1

Refer to the circuit shown in Figure 1.

- (a) Calculate R_T , I_1 and V_1 . (7 marks)
- (b) Use any method that you know to solve for I_2 , I_3 , I_4 , V_2 , V_3 and V_4 . (12 marks)
- (c) Calculate the power dissipated at resistor R_4 . (2 marks)
- (d) Relate the value of current I_3 and I_4 with the value of resistance R_3 and R_4 shown in the circuit. (2 marks)
- (e) Relate the value of V_2 , V_3 and V_4 to the type of connection for resistors R_2 , R_3 and R_4 shown in the circuit. (2 marks)

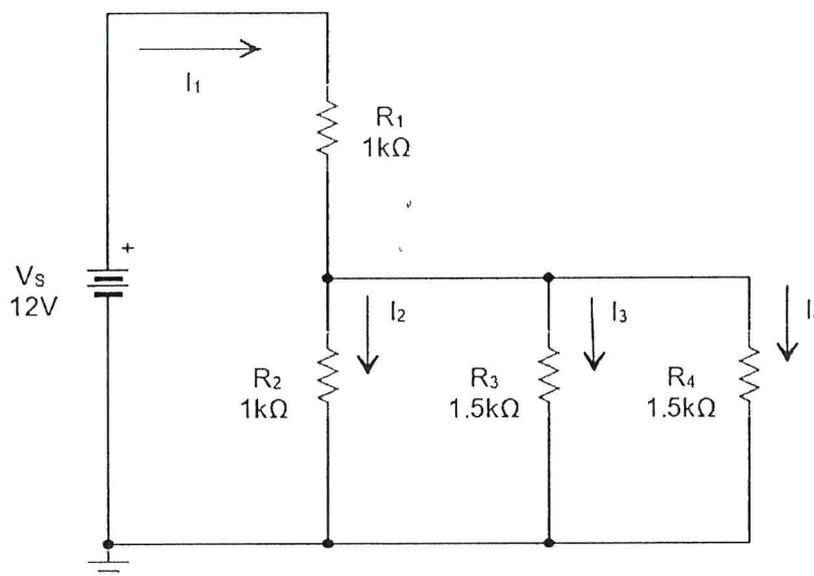


Figure 1: Resistive Network

Question 2

There are two meshes in the circuitry as shown in Figure 2.

- (a) Solving two meshes using Mesh Current Analysis method to solve for I_1 and I_2 . Then calculate the value of voltages across R_1 , R_2 and R_3 .

(18 marks)

- (b) The flow of electric current traverses resistor R_3 , which is the result of the combination of currents I_1 and I_2 . In order to obtain the voltage across resistor R_3 , it is necessary to establish a connection between Ohm's Law and the currents I_1 and I_2 . Redraw the circuit diagram and show the values of the currents flowing through each component and the voltages across resistors R_1 , R_2 , and R_3 .

(7 marks)


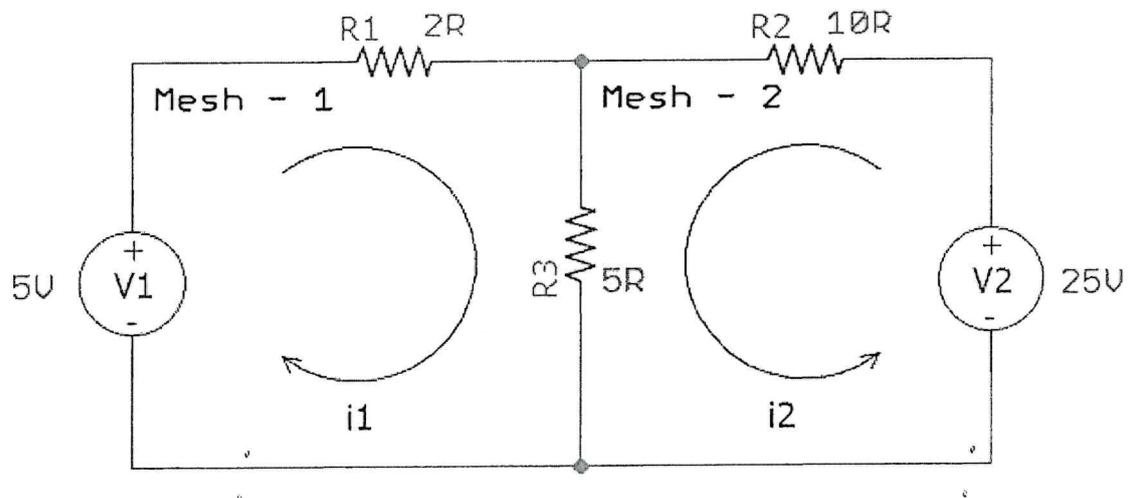


Figure 2: Resistive Network

Question 3

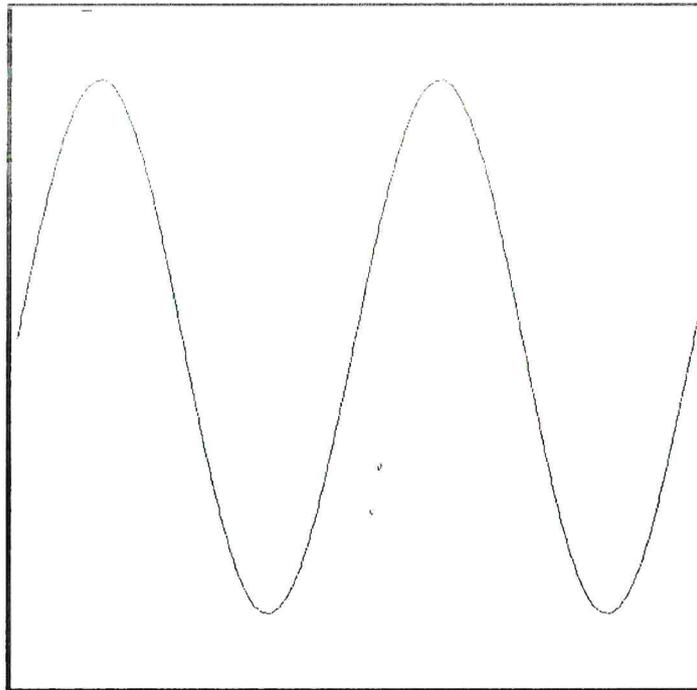- (a) A sinusoidal waveform on the oscilloscope screen is displayed in Figure 3. Show the calculation steps for the following magnitudes and the appropriate unit for each magnitude.
- period
 - frequency
 - peak value
 - peak-to-peak value
 - root-mean square (effective) value
 - average value
 - Describe the difference between root-mean square value and average value obtained from part (v) and part (vi) above by relating your answer to the appropriate formula.



Horizontal Setting: $500\mu\text{s}/\text{div}$
Vertical Setting: $2\text{V}/\text{div}$

Figure 3: Sinusoidal Waveform

(16 marks)

- (b) Consider the circuit shown in Figure 4. By using any appropriate method prove that the voltage V_b across resistor R_3 has a value of 24 volts.

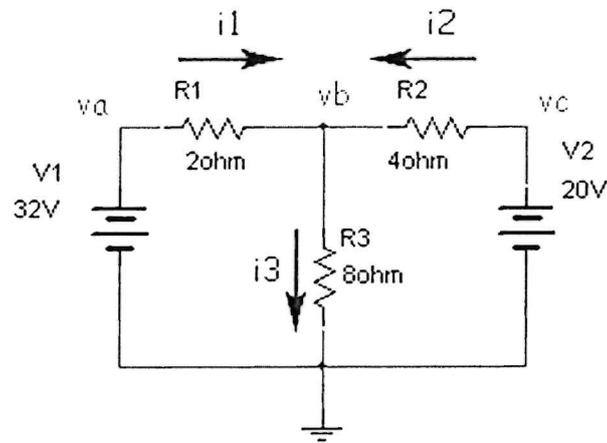


Figure 4: Resistive Circuit Network

(9 marks)

Question 4

Figure 5 shows a series RLC circuit containing a resistance of 12Ω , an inductance of 0.15H and a capacitor of $100\mu\text{F}$ are connected in series across a 100V , 50Hz supply. Calculate the following magnitudes:

- Total impedance
- Current in the circuit
- Total voltage across the resistor
- Total voltage across the inductor
- Total voltage across the capacitor
- True Power
- Apparent power
- Power factor
- Sketch the voltage phasor diagram

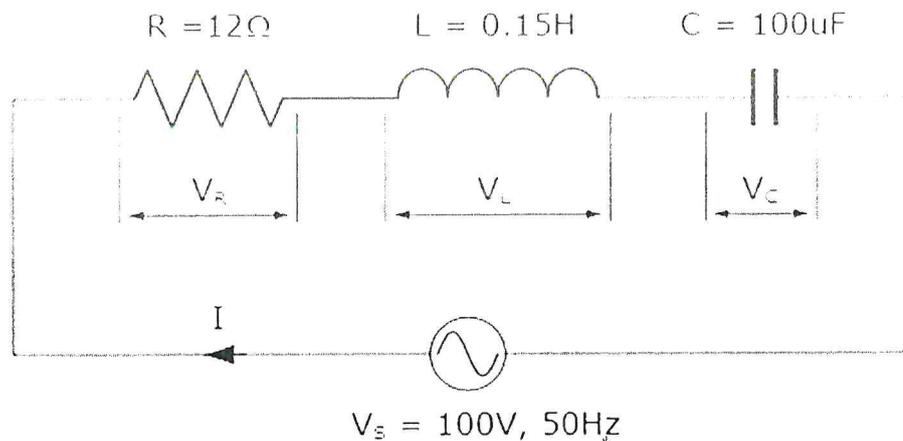


Figure 5: RLC Network

(25 marks)

END OF QUESTION PAPER

FORMULA SHEET

$$V = \frac{W}{Q}$$

$$W = F \times d$$

$$I = \frac{Q}{t}$$

$$P = \frac{W}{t}$$

$$V = I \times R$$

$$P = V \times I$$

$$R_T = R_1 + R_2 + R_3 + \dots R_n$$

$$V_x = \frac{R_x}{R_T} \times V_T$$

$$\sum V = V_s - V_1 - V_2 - V_3 - \dots V_n$$

$$P_T = P_1 + P_2 + P_3 + \dots P_n$$

$$P = I^2 \times R$$

$$P = \frac{V^2}{R}$$

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots \frac{1}{R_n}$$

$$I_x = \frac{R_T}{R_x} \times I_T$$

$$\sum I = I_s - I_1 - I_2 - I_3 - \dots I_n$$

$$V_{pp} = 2 \times V_p$$

$$f = \frac{1}{T}$$

$$V_{rms} = \frac{V_p}{\sqrt{2}}$$

$$V_{ave} = \frac{2 \times V_p}{\pi}$$

$$C = \frac{Q}{V}$$

$$C_T = C_1 + C_2 + C_3 + \dots C_n$$

$$X_C = \frac{1}{2\pi f C}$$

$$Z = \sqrt{R^2 + X_C^2}$$

$$V = I \times Z$$

$$Q = C \times V$$

$$\frac{1}{C_T} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \frac{1}{C_n}$$

$$\theta = \tan^{-1} \left(\frac{-X_C}{R} \right)$$

$$V_T = \sqrt{V_R^2 + V_C^2}$$

$$V_C = I \times X_C$$

FORMULA SHEET

$$L_T = L_1 + L_2 + L_3 + \dots L_n$$

$$X_L = 2\pi fL$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$V_L = I \times X_L$$

$$\frac{1}{L_T} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \dots \frac{1}{L_n}$$

$$\theta = \tan^{-1} \left(\frac{-X_L}{R} \right)$$

$$V_T = \sqrt{V_R^2 + V_L^2}$$

$$X_{tot} = |X_L - X_C|$$

$$\theta = \tan^{-1} \left(\frac{X_{tot}}{R} \right)$$

$$P_{reactive} = V \times I \sin \theta$$

$$Z_{tot} = \sqrt{R^2 + X_{tot}^2}$$

$$P_{true} = V \times I \cos \theta$$

$$P_{apparent} = V \times I$$

