



**UNIVERSITI KUALA LUMPUR
Malaysia France Institute**

**FINAL EXAMINATION
SEPTEMBER 2013 SESSION**

SUBJECT CODE : FED 10103
SUBJECT TITLE : ELECTRICAL FUNDAMENTAL
LEVEL : DIPLOMA
TIME / DURATION : 2.5 HOURS
DATE :

INSTRUCTIONS TO CANDIDATE

1. Please read the instructions given in the question paper **CAREFULLY**.
 2. This question paper is printed on both sides of the paper.
 3. Please write your answers on the answer booklet provided.
 4. Answers should be written in blue or black ink except for sketching, graphic and illustration.
 5. This question paper consists of **TWO (2)** sections. Section A and B. Answer all questions in Section A. For Section B, answer two (2) questions only.
 6. Answer all questions in English.
-

THERE ARE 5 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.

SECTION A (Total: 60 marks)

INSTRUCTION: Answer ALL questions.
Please use the answer booklet provided.

Question 1

(a) Identify the four-band color code of the following resistors

No.	Value	
1	$3.3 \times 10^3 \Omega \pm 10\%$	
2	$100 \Omega \pm 5\%$	
3	$88 \text{ M}\Omega \pm 10\%$	(6 marks)

(b) Explain briefly Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL) (6 marks)

(c) Define voltage, V and current, I , and state their units (6 marks)

Question 2

In **Figure 1**, determine the equivalent resistance, R_{eq} seen by the current source 10A, the current, I and the voltage, V .

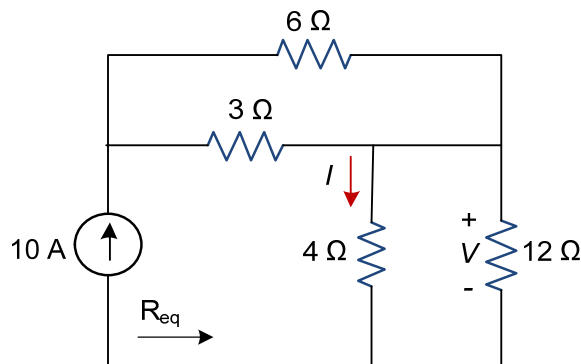


Figure 1

(10 marks)

Question 3

Based on the circuit shown in **Figure 2**, fill up **Table 1** with the related values of voltage, current, resistance, and power dissipated. Show all your works. (**Submit this page**).

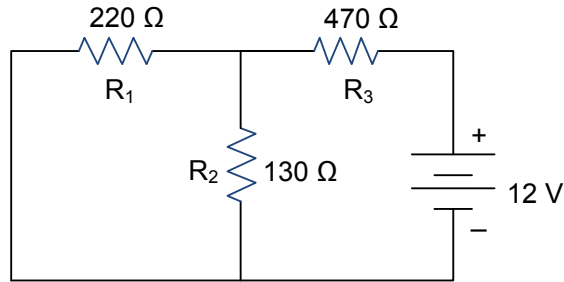


Figure 2

Table 1

	R ₁	R ₂	R ₃	TOTAL
Voltage, V				
Current, I				
Resistor, R	220 Ω	130 Ω	470 Ω	
Power, P				

(16 marks)

Question 4

Apply the superposition theorem on **Figure 3** and determine the voltage, v and the current through resistor $4\text{ k}\Omega$. Indicate the current direction.

(16 marks)

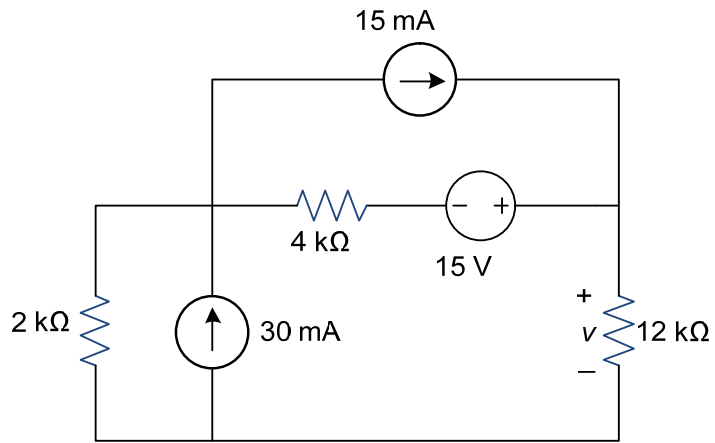


Figure 3

SECTION B (Total: 40 marks)

INSTRUCTION: Answer only TWO (2) questions

Please use the answer booklet provided.

Question 5

Based on the circuit in **Figure 4**, determine:

- (a) the Thevenin equivalent at the terminal of resistor R so that the maximum power is transferred (12 marks)
- (b) the relationship between R and Thevenin resistance, R_{TH} (3 marks)
- (c) the maximum power transferred to resistor, R (5 marks)

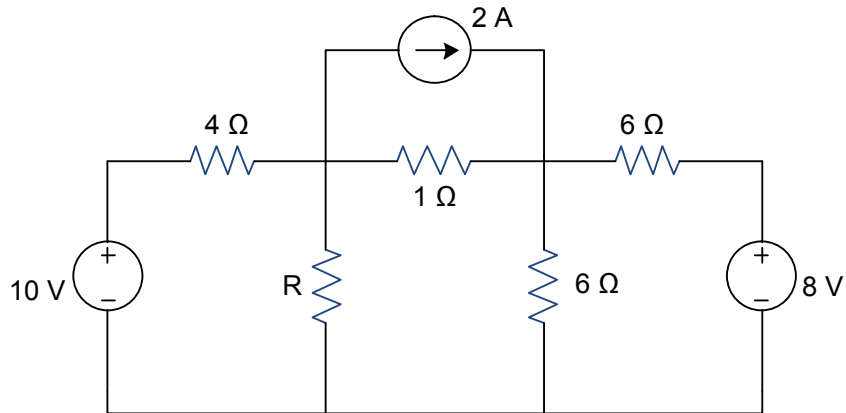


Figure 4

Question 6

Based on **Figure 5**, determine:

- (a) the current, i_x using nodal analysis. (14 marks)
- (b) the power supplied by the 4A current source (6 marks)

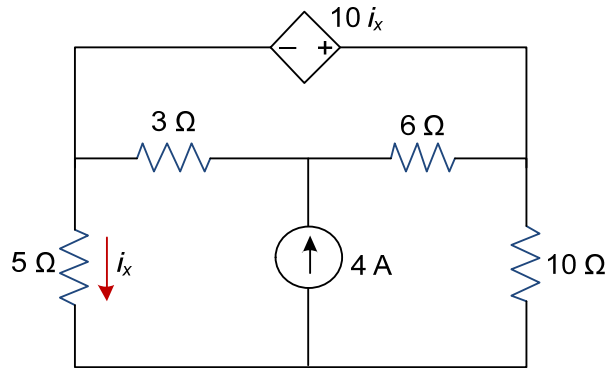


Figure 5

Question 7

By using mesh analysis on **Figure 6**, determine:

- (a) the voltage, V_x (15 marks)
- (b) the current through the resistor 10Ω (magnitude and direction) (5 marks)

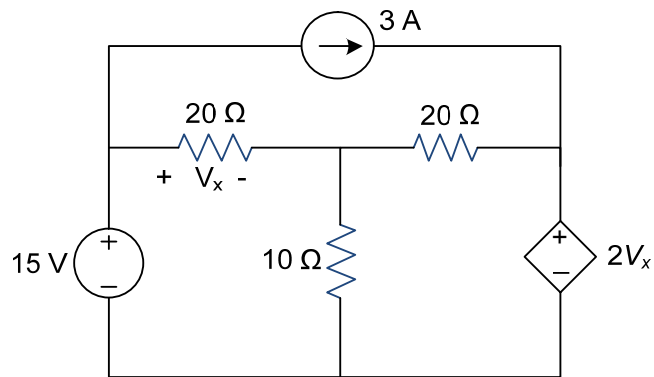


Figure 6

END OF QUESTION PAPER