



**UNIVERSITI KUALA LUMPUR
Malaysia France Institute**

**FINAL EXAMINATION
SEPTEMBER 2013 SESSION**

SUBJECT CODE : FLD 10202
SUBJECT TITLE : INSTRUMENTATION
LEVEL : DIPLOMA
TIME / DURATION : 2 HOURS
DATE :

INSTRUCTIONS TO CANDIDATES

1. Please read the instructions given in the question paper **CAREFULLY**.
2. This question paper is printed on both sides of the paper.
3. Please write your answers on the answer booklet provided.
4. Answers should be written in blue or black ink except for sketching, graphic and illustration.
5. This question paper consists of **TWO (2)** sections. Section A and B. Answer all questions in Section A. For Section B, answer two (2) questions only.
6. Answer all questions in English.

THERE ARE 8 PAGES OF QUESTIONS, EXCLUDING THIS PAGE AND APPENDIX.

SECTION A (Total: 60 marks)

INSTRUCTION: Answer ALL questions.
Please use the answer booklet provided.

Question 1

- (a) State the **three (3)** major categories of error and give one example each.
(6 marks)
- (b) The following set of data is obtained from an instrument for a particular measurement.

Table 1

Data	X_1	X_2	X_3	X_4	X_5	X_6
Measured value	30.7	31.1	31.2	30.6	30.7	31.3

Determine:

- (i) The arithmetic mean.
(2 marks)
- (ii) The deviation of each value.
(6 marks)
- (iii) The average deviation for the data.
(3 marks)
- (iv) The standard deviation for the data.
(3 marks)

Question 2

- (a) State **four (4)** possible measurements that can be performed by using C.R.O (Cathode Ray Oscilloscope).
(4 marks)
- (b) List out the **four (4)** groups of front control panel of a C.R.O.
(4 marks)
- (c) State **three (3)** standard waveforms that can be delivered by a function generator.
(3 marks)
- (d) In an experiment, a function generator is used to generate a sinusoidal waveform of 1 kHz, $14V_{PP}$. An oscilloscope (C.R.O) is used to display the waveform with the vertical scale set to 2V/div and the horizontal scale set to 0.5ms/div respectively.
- (i) Draw the waveform on the C.R.O screen shown in **Figure 1**.
(6 marks)
- (ii) Calculate the root-mean-square/effective value of the sinusoidal waveform, V_{RMS} .
(3 marks)

Answer for question 2(d)i.

(ATTACH THIS PAPER TOGETHER WITH THE ANSWER BOOKLET)

ID Number: _____

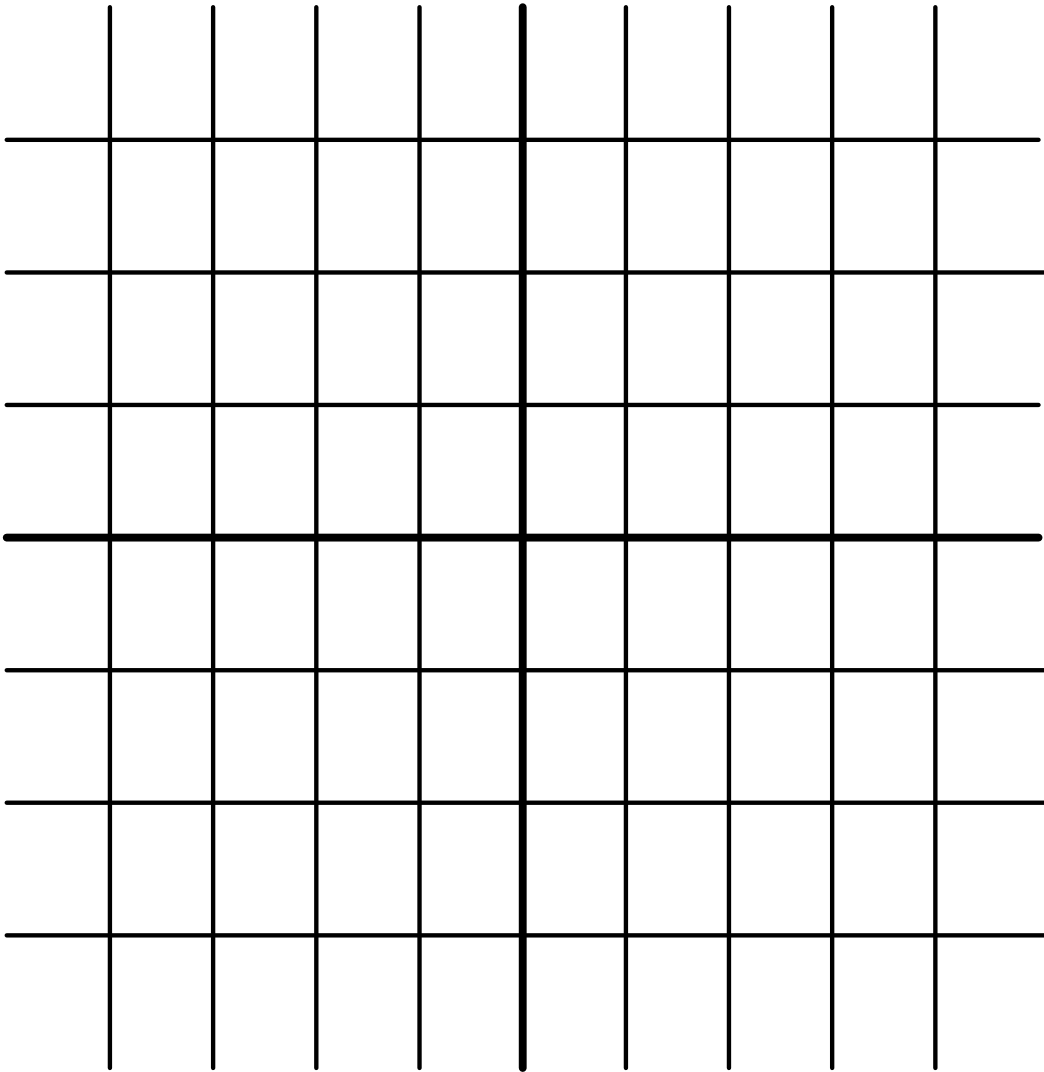


Figure 1

Question 3

(a) **Figure 2** shows an *Electrodynamometer*. Based on **Figure 2**:

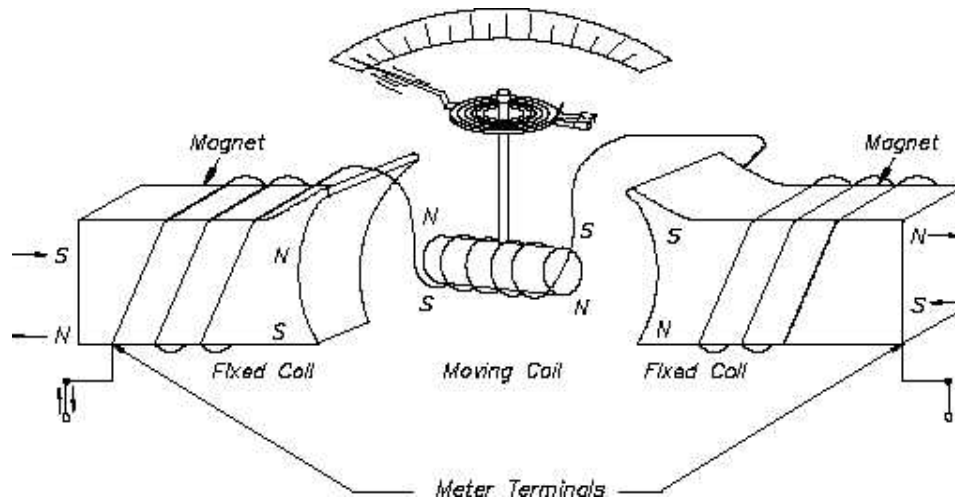


Figure 2

- (i) Explain the basic principle of this instrument. (4 marks)
- (ii) List out **two (2)** advantages and disadvantages of this instrument. (4 marks)

(b) The following questions refer to the instrument shown in **Figure 3**.

(i) Identify the instrument. (1 mark)

(ii) State **one (1)** difference between this instrument and moving iron types instrument.

(2 marks)

(iii) The instrument has the following data:

Number of turns = 150

Width of the coil = 15mm

Length of the coil = 31mm

Flux density in the gap = 0.2 Wb/m^2

Calculate the deflecting torque when carrying a current of 30mA and the deflection, if the control spring constant is $2 \times 10^{-6} \text{ Nm/Degree}$.

(9 marks)

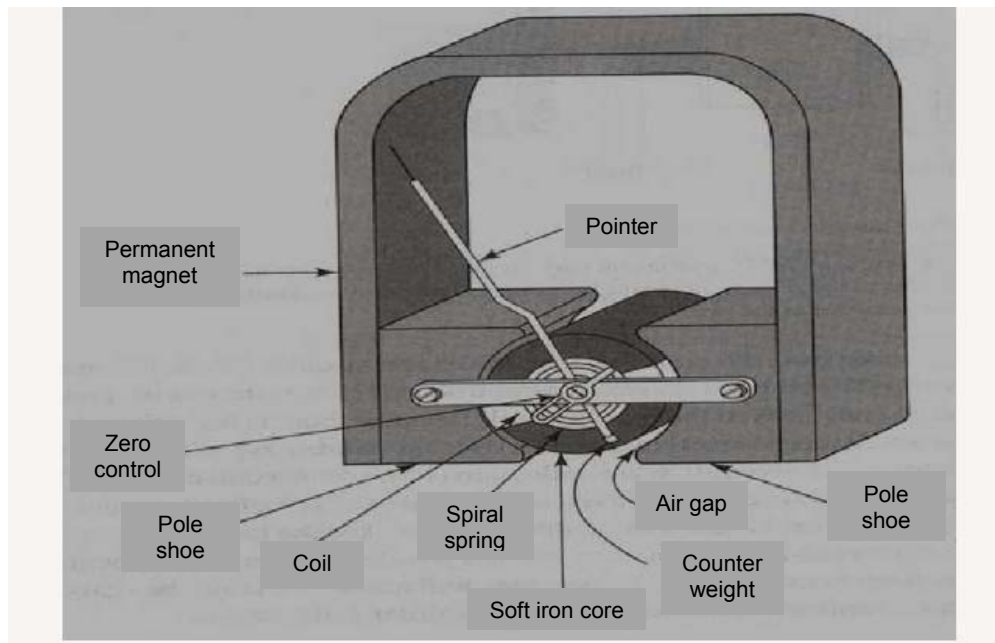


Figure 3

SECTION B (Total: 40 marks)**INSTRUCTION: Answer only TWO (2) questions.****Please use the answer booklet provided.****Question 4**

(a) Design a multirange DC miliammeter with a basic meter having a resistance 70Ω and full scale deflection for the current of 3mA . The required ranges are $0\text{-}10\text{ mA}$, $0\text{-}25\text{ mA}$ and $0\text{-}50\text{ mA}$. Your design should provide the following:

(i) The value of shunt resistance for each range.

(8 marks)

(ii) The multirange miliammeter circuit.

(2 marks)

(b) A basic D'Arsonval movement meter with an internal resistance of $40\ \Omega$ and full scale deflection current of 4mA is to be used as a multirange voltmeter. Design the series string of multipliers to obtain the voltage ranges of $0\text{-}10\text{V}$, $0\text{-}100\text{V}$, $0\text{-}300\text{V}$ and $0\text{-}500\text{V}$.

(10 marks)

Question 5

- (a) Meter A has a range of 0-100V and multiplier resistance of 20k Ω . Meter B has a range 0-1000V and a multiplier resistance of 200k Ω . Both meters have basic meter resistance of 2k Ω . Which meter is more sensitive?

(5 marks)

- (b) A D'Arsonval movement having an internal resistance of 100 Ω and full scale current of 50 μ A is used.

- (i) Design an Aryton shunt to provide an ammeter with current ranges of 0 – 1mA, 0-10mA and 0-100mA.

(13 marks)

- (ii) Draw the circuit of the Aryton shunt ammeter in part b(i).

(2 marks)

Question 6

- (a) There are **two (2)** types of Bridge circuits; DC bridges and AC bridges. Briefly explain the differences between them. (4 marks)

- (b) List out **two (2)** major applications of the Wheatstone's bridge. (4 marks)

- (c) An unbalanced Wheatstone bridge is given in **Figure 4**. Calculate the current through the galvanometer. (12 marks)

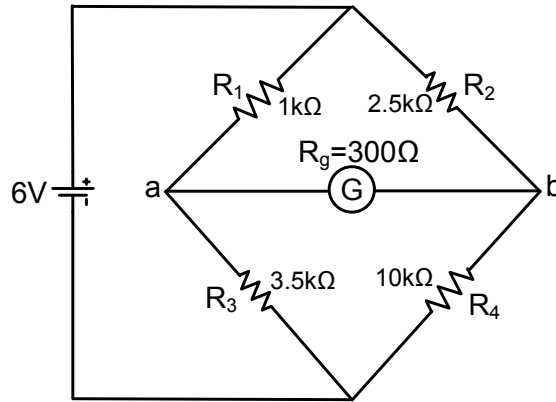


Figure 4

END OF QUESTION PAPER

APPENDIX

FORMULA

1. $V_P = (\sqrt{2})(V_{RMS})$

2. Arithmetic mean, $\bar{x} = \frac{x_1 + x_2 + \dots + x_n}{n}$

3. Deviation, $d_n = x_n - \bar{x}$

4. Average Deviation, $D_{av} = \frac{|d_1| + \dots + |d_n|}{n}$

5. Standard Deviation, $\sigma = \sqrt{\frac{d_1^2 + d_2^2 + \dots + d_n^2}{n-1}}$

6. Precision = $1 - \left| \frac{X_n - \bar{X}_n}{\bar{X}_n} \right|$

7. Deflecting torque, $\tau_d = BxAxNxI$

8. Deflecting torque, $\tau_d = K\theta$

9. Accuracy, $A = 1 - \left| \frac{Y_n - X_n}{Y_n} \right|$

10. Ayrton Shunt Formula: $I_{sh}R_{sh} = I_m R_m$

11. Series Type Ohmmeter Formula: $R_1 = R_h - \frac{I_{fsd} x R_m x R_h}{V}$ and

$$R_2 = \frac{I_{fsd} x R_m x R_h}{V - (I_{fsd} x R_h)}$$