



UNIVERSITI KUALA LUMPUR
Malaysia France Institute

FINAL EXAMINATION

SEPTEMBER 2014 SESSION

SUBJECT CODE : FLB12013 / FLB12023
SUBJECT TITLE : ANALOG ELECTRONICS
LEVEL : BACHELOR
TIME / DURATION : 3.30 PM – 6.00 PM
(2.5 HOURS)
DATE : 08 JANUARY 2015


INSTRUCTIONS TO CANDIDATES

1. Please read the instructions given in the question paper **CAREFULLY**.
 2. This question paper is printed on both sides of the paper.
 3. Please write your answers on the answer booklet provided.
 4. Answers should be written in blue or black ink except for sketching, graphic and illustration.
 5. This question paper consists of **TWO (2) sections**. Section A and B. Answer all questions in Section A. For Section B, answer three (3) questions only.
 6. Answer all questions in English.
 7. Do not open the question paper until instructed to do so
-

THERE ARE 6 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.

SECTION A (Total: 40 marks)**INSTRUCTION: Answer ALL questions.****Please use the answer booklet provided.****Question 1**

- (a) Define:
- (i) Intrinsic material (2 marks)
 - (ii) Extrinsic material (2 marks)
- (b) Briefly explain the formation of:
- (i) N-type materials (3 marks)
 - (ii) P-type materials (3 marks)
- (c) Refer to **Figure 1**, determine:
- (i) The current, I (4 marks)
 - (ii) The output voltage at V_{o1} and V_{o2} (6 marks)

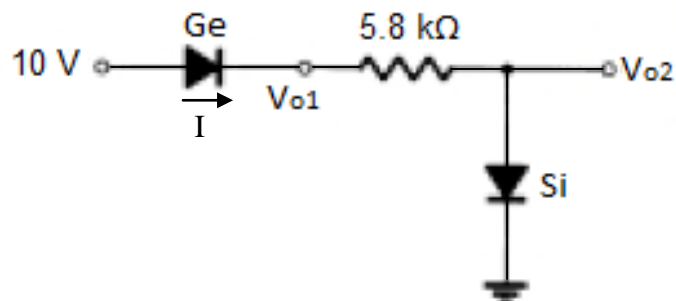**Figure 1**

Question 2

(a) **Figure 2** shows a half-wave rectifier with a silicon diode.

- (i) Determine the output voltage, V_o (3 marks)
- (ii) Sketch the output waveform (3 marks)
- (iii) Calculate the average output voltage, V_{dc} (3 marks)

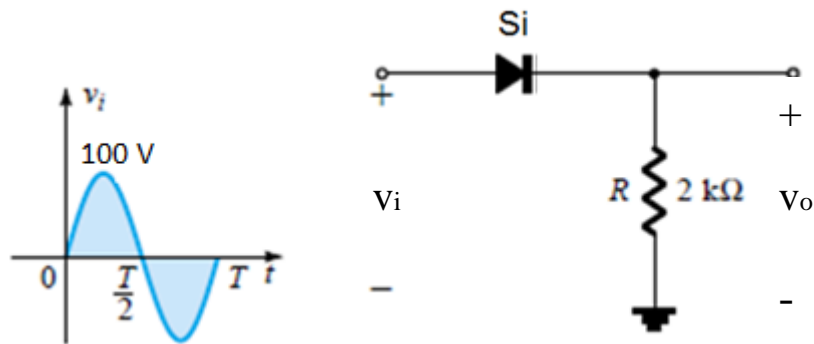


Figure 2

(b) **Figure 3** shows a full-wave rectifier with silicon diodes.

- (i) Determine the output voltage, V_o (5 marks)
- (ii) Sketch the output waveform (3 marks)
- (iii) Calculate the average output voltage, V_{dc} (3 marks)

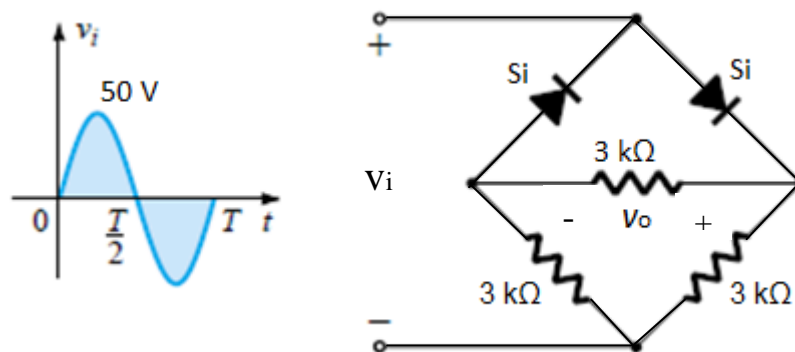
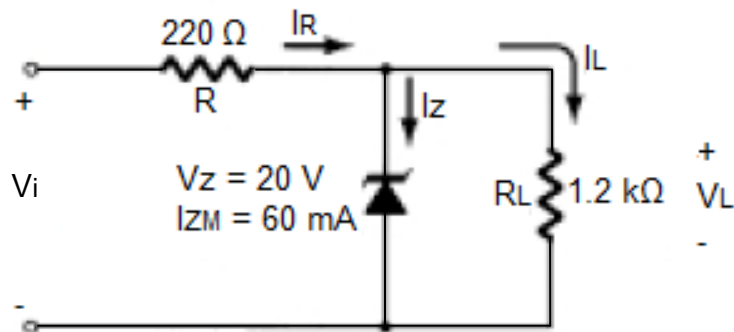


Figure 3

SECTION B (Total: 60 marks)**INSTRUCTION: Answer THREE (3) questions only.****Please use the answer booklet provided.****Question 3****Figure 4** shows a regulator network of a Zener diode.

- (a) Determine V_{\min} , I_L , $I_{R_{\max}}$ and V_{\max} that will maintain the Zener diode in the “on” state (14 marks)
- (b) Calculate the maximum wattage rating of the Zener diode (3 marks)
- (c) Sketch a plot of V_L versus V_i . (3 marks)

**Figure 4**

Question 4

(a) List two (2) basic types of transistor. (2 marks)

(b) Refer to fixed-bias configuration in **Figure 5**, given $R_C = 2.2\text{ k}\Omega$, $I_B = 20\text{ }\mu\text{A}$, $I_E = 4\text{ mA}$ and $V_{CE} = 7.2\text{ V}$. Determine:

(i) V_{BE} and V_E (3 marks)

(ii) I_C (3 marks)

(iii) V_{CC} (3 marks)

(iv) β (3 marks)

(v) R_B (3 marks)

(vi) I_{Csat} (3 marks)

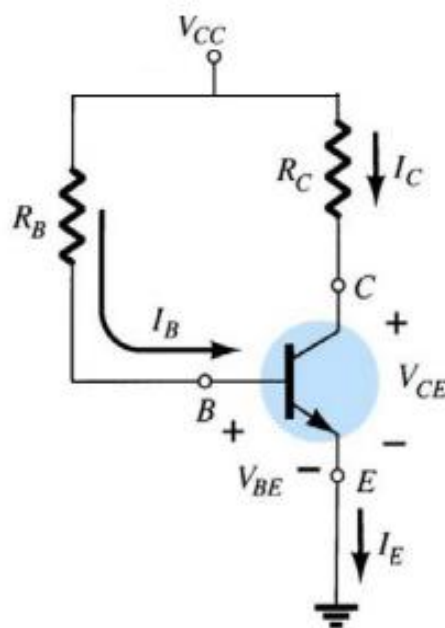


Figure 5

Question 5

Refer to the emitter-stabilized bias circuit in **Figure 6**, calculate:

- (a) I_E (3 marks)
- (b) β (3 marks)
- (c) V_{CC} (5 marks)
- (d) R_B (5 marks)
- (e) I_{Csat} (4 marks)

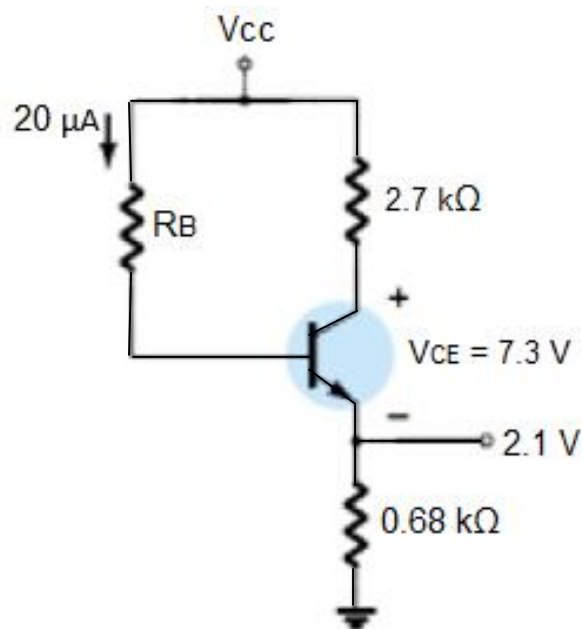


Figure 6

Question 6

- (a) Calculate V_o for the circuit shown in **Figure 7**: (10 marks)

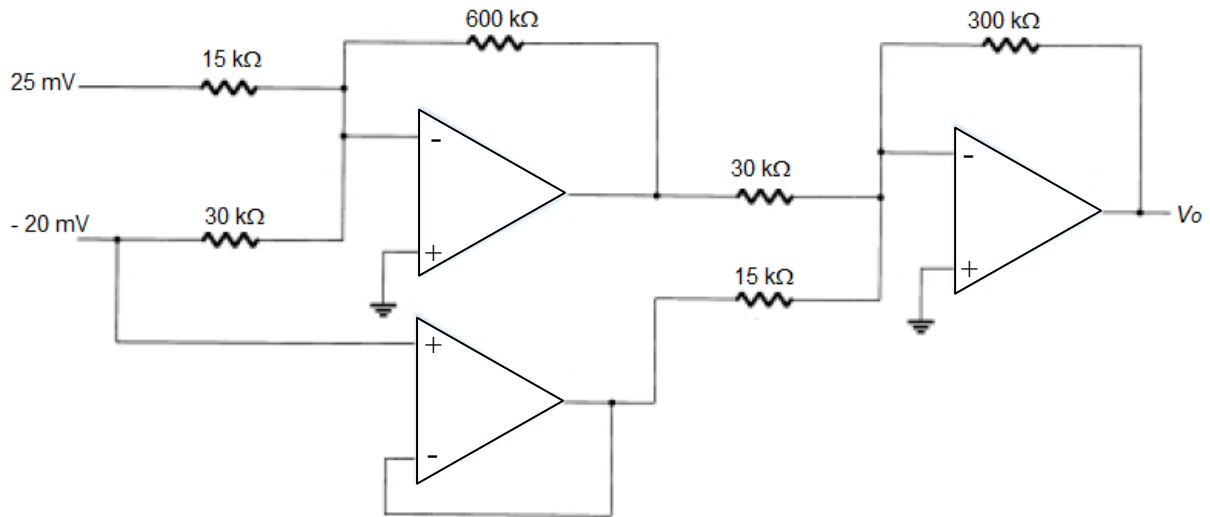


Figure 7

- (b) Design a first order low pass filter which enable to filter the signal above 1.5 kHz with a voltage gain of 6. Given $R_G = 10\text{ k}\Omega$ and capacitor, $C_1 = 0.05\text{ }\mu\text{F}$. (10 marks)

END OF QUESTION PAPER