



**UNIVERSITI KUALA LUMPUR**  
**KAMPUS CAWANGAN MALAYSIAN SPANISH INSTITUTE**

---

---

**FINAL EXAMINATION**

**OCTOBER 2025 SEMESTER**

---

---

**COURSE CODE** : SAB24803  
**COURSE NAME** : ANALOG CIRCUIT APPLICATIONS 2  
**PROGRAMME LEVEL** : BACHELOR  
**DATE** : 30 JANUARY 2026  
**TIME** : 9.00AM – 12.00PM  
**DURATION** : 3 HOURS

---

**INSTRUCTIONS TO CANDIDATES**

---

1. Please **CAREFULLY** read the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **FIVE (5)** questions. Answer **FOUR (4)** questions **ONLY**.
4. Answer all questions in English language **ONLY**.

---

**THERE ARE 5 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.**

---



Question 1

Figure 1 shows the energy band diagrams of Semiconductors A, B, and C.  $E_C$ ,  $E_V$ , and  $E_{Fi}$  are the conduction bands, valence bands, and intrinsic Fermi level, respectively.  $E_D$  is the donor level and  $E_A$  is the acceptor level. Based on the figure, answer the following questions:

 


Figure 1 Energy band diagram.

- State the type of Semiconductor A, B, and C. (5 marks)
- Determine the majority and minority carriers of Semiconductors B and C, respectively. (8 marks)
- Define the Z-process as shown in Figure 1. Then, briefly explain the formation of Semiconductors B and C. Assume that Semiconductor A is Silicon. (12 marks)

Question 2

- a) For ideal diodes, show the voltage waveforms across the secondary winding and across  $R_L$  when a  $230\text{ V}_{\text{rms}}$  sine wave is applied to the primary winding in Figure 2.

(10 marks)

- b) What is minimum peak inversion voltage (PIV) rating must the diode have?

(5 marks)

 


Figure 2 A centre-tapped full-wave rectifier.

- c) Figure 3 shows a basic Zener diode regulator circuit. What is the smallest load resistor that can be used before losing regulation? Assume an ideal Zener diode model and  $V_{\text{IN}} = 20\text{ V}$ .

 


Figure 3 A basic Zener diode regulator circuit.

(10 marks)

## Question 3

Figure 4 shows an npn bipolar junction transistor (BJT) in a simple circuit. In this configuration, the transistor is biased in active mode and has a current gain of  $\beta_{DC} = 50$ . The BJT is of Silicon with  $V_{BE} = 0.7$  V. Given  $I_B = 0.1$  mA.

 


Figure 4 An npn BJT in a common-emitter circuit configuration.

- For the transistor circuit in Figure 4, what is  $V_{CE}$  when  $V_{BB} = 0$  V. (4 marks)
- What is the saturation current of the BJT circuit? Neglect  $V_{CE(sat)}$ . (4 marks)
- Is the transistor saturated? Justify. (2 marks)
- Plot the DC load line of the transistor circuit and determine its operating point (Q-point). (15 marks)

## Question 4

Figure 5 shows a common emitter amplifier with a voltage divider biasing. The common emitter amplifier has a variable gain control, using a  $150\ \Omega$  potentiometer for  $R_E$  with the wiper ac grounded. As the potentiometer is adjusted, more or less of  $R_E$  is bypassed to the ground at the signal frequency, thus varying the gain. The total  $R_E$  remains constant to dc because the capacitor is an open to dc, keeping the bias fixed. Given  $V_T = 26\ \text{mV}$  at room temperature and  $V_A = 100\ \text{V}$ .

 


Figure 5 A common emitter amplifier with a voltage divider biasing circuit.

- a) Determine the maximum and the minimum gain for the amplifier.

(20 marks)

- b) If a load resistance of  $600\ \Omega$  is placed on the output of the amplifier in Figure 5, what is the maximum gain?

(5 marks)

**Question 5**

An n-channel enhancement mode Metal Oxide Semiconductor Field Effect Transistor (MOSFET) operating with  $V_{GS} = 1.5 \text{ V}$  and  $V_{DS} = 2.0 \text{ V}$  has the following parameters:

Oxide thickness: 15 nm  
Electron mobility:  $450 \text{ cm}^2/\text{V}\cdot\text{s}$   
Threshold voltage: 0.7 V  
Width-to-length (W/L) ratio: 30

- a) Determine whether the MOSFET is operating in the saturation or non-saturation region.  
(2 marks)
- b) Calculate the drain current,  $I_D$ .  
(10 marks)
- c) If the channel length modulation parameter  $\lambda = 0.03 \text{ V}^{-1}$ , determine the corrected drain current  $I_D$  taking into account the channel length modulation.  
(10 marks)
- d) Compare the answers obtained in (b) and (c), and explain the difference.  
(3 marks)

**END OF EXAMINATION PAPER**

