



UNIVERSITI KUALA LUMPUR
Malaysian Institute of Marine Engineering Technology

FINAL EXAMINATION
JULY 2025 SEMESTER SESSION

SUBJECT CODE : LED31403

SUBJECT TITLE : POWER ELECTRONICS AND DEVICES

PROGRAMME NAME : DIPLOMA OF ENGINEERING TECHNOLOGY IN
(FOR MPU: PROGRAMME LEVEL) ELECTRICAL AND ELECTRONICS (MARINE)

TIME / DURATION : 09.00 AM - 12.00 PM
(3 HOURS)

DATE : 23 DECEMBER 2025

INSTRUCTIONS TO CANDIDATES

1. Please read **CAREFULLY** the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **TWO (2)** sections; Section A and Section B.
4. Answer **ALL** questions in Section A. For Section A, answer **TWO (2)** questions **ONLY**.
5. Please write your answers on this answer booklet provided.
6. Answer **ALL** questions in English language **ONLY**.
7. Answer should be written in blue or black ink except for sketching, graphic and illustrations.

THERE ARE 6 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.

SECTION A (Total:60 marks)

INSTRUCTION: Answer ALL questions

Please use the answer booklet provided

Question 1

With reference to introduction of power electronics

(a) State the definition of power electronics and give 2 examples of its application. The 2 examples of power devices are DIODE and TRIAC. Draw their symbol and characteristic.

(6 marks)

(b) 4 types of power electronics circuit are listed below. Explain each circuit function in terms of electric power conversion.

- i. Rectifier
- ii. AC voltage controller.
- iii. DC chopper.
- iv. Inverter.

(4 marks)

(c) Thyristor is one of the most important types of semiconductor devices. Draw the symbol and the construction of 3 p-n junctions.

Draw the thyristor characteristics graph and show the followings:

- i. Forward Breakover Voltage, V_{BO} .
- ii. Reverse Breakdown Voltage, V_{RB} .
- iii. Latching Current, I_L .
- iv. Holding current, I_H .
- v. Gate Triggered Curve.

(10 marks)

Question 2

With reference to AC to DC converter

- (a) With the aid of suitable circuit, explain briefly the operation of the uncontrolled half-wave rectifier with R load (4 marks)
- (b) Sketch the waveform of the input voltage, V_s , output voltage, V_o and input current i_s and voltage across the diode, V_D for the circuit in part (a). (6 marks)
- (c) A uncontrolled half wave rectifier has an AC source of $100\sqrt{2} V_{rms}$ at 50 Hz. The load is 100Ω resistors. Determine:
- i. the dc output voltage (4 marks)
 - ii. the dc load current (2 marks)
 - iii. the ac load current (2 marks)
 - iv. the input power to the rectifier (2 marks)

Question 3

With reference to DC-to-DC converter

- (a) State the function of buck converter and boost converter. (2 marks)
- (b) Sketch circuit diagrams for buck converter and boost converter. Label important parameters in the circuits. (4 marks)
- (c) A buck converter with parameters $L = 10\text{mH}$, $C = 50\mu\text{F}$ and $R = 5\Omega$ is supplied with 24V input and operated with 0.6 duty ratio. Its switching frequency is 150 kHz. Calculate:
- i. the output voltage, (2 marks)
 - ii. the maximum and minimum inductor current. (2 marks)
- (d) A boost converter with a 5 mH inductor has an input of 50V and an output of 125 V. the switching frequency is 4 kHz and the output power to the resistor load is 125W. calculate :
- i. the duty cycle, (3 marks)
 - ii. the minimum and maximum inductor current (4 marks)
 - iii. sketch the inductor current waveform over one (1) period. Mark the minimum and maximum values of inductor current based calculation made in Part:(d) (i). (3 marks)

SECTION B (Total:40 marks)

Question 2

INSTRUCTION: Answer only TWO (2) questions.

Please use the answer booklet provided.

Question 4

With reference to the AC to AC converter

(a) With the aid of suitable circuit explain briefly the operation of a single phase AC voltage controller with resistive load

(4 marks)

(b) Sketch the waveform of the input voltage, V_s output voltage, V_o and output current i_o and voltage across the switch, V_{sw} for the circuit in part (a).

(6 marks)

(c) The single phase AC voltage controller in Figure part (a) has a $120V_{rms}$ at 50 Hz source. The load resistance is 15Ω . The delay angle α is 90° Determine:

i. the rms source current to deliver 500W to the load

(4marks)

ii. the rms and average currents in the SCRs,

(4 marks)

iii. the power factor

(2 marks)

Question 5

With reference to the AC to DC converter

Controlled rectifier, which is also known as ac-dc converters are used especially in variable speed drives. Three phase controlled rectifiers are simple and less expensive and the efficiency is in general above 95%.

(a) Draw the circuits for the following single-phase controlled rectifiers below:

- i. Half-wave converter
- ii. Full-wave converter.

(b) A single phase full-wave converter is operated from 120V 50Hz supply. The circuit has a highly inductive load and following formulas are given:

$$V_{dc} = (2V_m \cos \alpha) / \pi$$

$$V_{rms} = V_s$$

The thyristors are fired at three different firing angles $\alpha : 0, \pi/2$ and π .

- i. Draw the input waveform to the circuit and draw the output waveforms for all firing angles.
- ii. Evaluate the following quantities and fill in the table below.

Quantity	$\alpha_1 = 0$	$\alpha_2 = \pi/2$	$\alpha_3 = \pi$
Average Output Voltage, V_{dc}			
RMS Output Voltage, V_{rms}			

(c) Conclude about the DC voltage of the full-wave converter.

(d) Give the application of this circuit.

(20 marks)

SECTION B (Total 40 marks)

NOTICE: Answer only TWO (2) questions.

Please use the answer booklet provided.

Question 6

With reference to the DC to AC converter

Question 6

With reference to the DC to AC converter

- a. DC to AC converter or inverter is one of the elements in power electronics. Explain the definition of inverter. Draw the block diagram and state 2 of their application.
- b. Draw the circuit of voltage source inverter and state the use of capacitor in the circuit.
- c. Draw the circuit of current source inverter and state the use of inductor in the circuit.
- d. Cycloconverter is one of type AC to AC converter. Draw the single phase circuit cycloconverter and sketch the input and output voltage across load.

(20 marks)

END OF QUESTION