



**UNIVERSITI KUALA LUMPUR**  
**Malaysian Institute of Marine Engineering Technology**

---

**FINAL EXAMINATION**  
**JULY 2025 SEMESTER SESSION**

---

<b>SUBJECT CODE</b>	<b>: LMD14103</b>
<b>SUBJECT TITLE</b>	<b>: FUNDAMENTAL OF ELECTRICAL AND ELECTRONICS TECHNOLOGY</b>
<b>PROGRAMME NAME</b> (FOR MPU: PROGRAMME LEVEL)	<b>: DIPLOMA OF ENGINEERING TECHNOLOGY IN MARINE ENGINEERING</b>
<b>TIME / DURATION</b>	<b>: 9.00 AM - 12.00 PM</b> <b>(3 HOURS)</b>
<b>DATE</b>	<b>: 22 DECEMBER 2025</b>

---

**INSTRUCTIONS TO CANDIDATES**

---

1. Please read **CAREFULLY** the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **TWO (2)** sections; Section A and Section B.
4. Answer **ALL** question in Section A, and **TWO (2)** questions **ONLY** in Section B.
5. Please write your answers on this answer booklet provided.
6. Answer **ALL** questions in English language **ONLY**.
7. Answer should be written in blue or black ink except for sketching, graphic and illustration.

---

**THERE ARE 4 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.**

---

## SECTION A (Total: 60 marks)

**INSTRUCTION: Answer ALL questions.**

**Please use the answer booklet provided.**

### Question 1

With reference to **Basic Electronics**:

During a class on Electronic Control Equipment for marine systems, the instructor presents examples of PLC-based automation, CPP control, and IACMS fuel monitoring.

- (a) Explain the main components of a Programmable Logic Controller (PLC). (6 marks)
- (b) Describe the control functions of a Controllable Pitch Propeller (CPP) control system. (8 marks)
- (c) Explain the works of an Integrated Automation Control and Monitoring System (IACMS) integrates sensor on fuel tank monitoring. (6 marks)

### Question 2

With reference to **DC Circuits**:

A 48 V DC supply from the ship's auxiliary battery powers a navigation aid circuit consisting of:

- $R_1 = 10 \Omega$  in series (current-limiting resistor)
- $R_2 = 20 \Omega$  representing the radar display heater (parallel branch)
- $R_3 = 30 \Omega$  representing the electronic chart display cooling fan (parallel branch)

The chief engineer must assess load distribution and determine a replacement heater value that maintains a specified fan voltage.

- (a) Identify the equivalent resistance of the circuit and the total current drawn from the 48 V battery. (6 marks)

- (b) Solve the followings:
- i. The voltage across the parallel devices (radar heater and cooling fan). (2 marks)
  - ii. The currents through  $R_2$  and  $R_3$ . (4 marks)
  - iii. The power dissipated by  $R_2$ . (2 marks)
- (c) If the radar display heater is replaced by new resistor value of  $R_2$  so that the voltage across the cooling fan ( $R_3$ ) becomes exactly 18 V, identify the new required value of this new resistor  $R_2$ . (6 marks)

### Question 3

With reference to **Magnetism**:

A ship's alternator operates based on electromagnetic induction principles.

- (a) Describe Lenz's Law. (6 marks)
- (b) Explain the application of Lenz's Law in the operation of an AC generator on board ship. (8 marks)
- (c) A coil with 50 turns experiences a change in magnetic flux from 0.06 Wb to 0.02 Wb in 0.2 seconds. Solve for the polarity of the induced voltage according to Lenz's Law and its magnitude. (6 marks)

**SECTION B (Total: 40 marks)****INSTRUCTION: Answer TWO (2) questions only.****Please use the answer booklet provided.****Question 4**With reference to **AC Circuits**:

A ship's refrigeration motor draws 40 A at 230 V with a power factor of 0.7 lagging.

- (a) Calculate the real power consumed. (6 marks)
- (b) Explain the undesirability of low power factor and its improvement using capacitors. (8 marks)
- (c) Calculate the apparent power and reactive power. (6 marks)

**Question 5**With reference to **AC Circuits**:A ship's communication radio has an LC tuning circuit with  $L = 5 \text{ mH}$  and  $C = 0.01 \text{ }\mu\text{F}$ .

- (a) Calculate the resonant frequency. (6 marks)
- (b) Explain the important of resonance in radio communication systems. (8 marks)
- (c) If the inductance is doubled, calculate the new resonant frequency. (6 marks)

**Question 6**

With reference to **AC Circuits**:

A three-phase induction motor on board is supplied at 400 V, 50 Hz, drawing 30 A at 0.85 power factor.

- (a) Calculate the real power output of the motor. (6 marks)
- (b) Explain the advantages of using three-phase power on ships compared to single-phase. (8 marks)
- (c) Calculate the apparent power and reactive power. (6 marks)

**END OF EXAMINATION PAPER**