



**UNIVERSITI KUALA LUMPUR**  
**Malaysian Institute of Marine Engineering Technology**

---

**FINAL EXAMINATION**  
**OCTOBER 2025 SEMESTER SESSION**

---

<b>SUBJECT CODE</b>	<b>: LEB22103</b>
<b>SUBJECT TITLE</b>	<b>: ELECTRICAL AND ELECTRONIC PRINCIPLES</b>
<b>PROGRAMME NAME</b> (FOR MPU: PROGRAMME LEVEL)	<b>: BACHELOR OF ELECTRICAL AND ELECTRONICS ENGINEERING TECHNOLOGY (MARINE) WITH HONOURS</b>
<b>TIME / DURATION</b>	<b>: 2.00 PM - 5.00 PM (3 HOURS)</b>
<b>DATE</b>	<b>: 26 JANUARY 2026</b>

---

**INSTRUCTIONS TO CANDIDATES**

---

1. Please read **CAREFULLY** the instructions given in the question paper.
  2. This question paper has information printed on both sides of the paper.
  3. This question paper consists of **TWO (2)** Sections, Section A and Section B.
  4. Answer **ALL** questions in Section A. For Section B, answer **THREE (3)** questions.
  5. Answer **ALL** questions in the answer booklet provided.
  6. Answer **ALL** questions in English language **ONLY**.
  7. Formula sheet has been appended for your reference.
- 

**THERE ARE 8 PAGES OF QUESTIONS, INCLUDING THIS PAGE.**

---

**SECTION A (Total: 40 marks)****INSTRUCTION: Answer ALL questions.****Question 1**

- (a) Define electric charge and electric current using the mathematical relationship between electric current and charge.  
(4 marks)
- (b) Describe the characteristics of series and parallel circuits in terms of voltage and current distribution.  
(4 marks)
- (c) Explain the principle of a magnetic field by stating **TWO (2)** characteristics of magnetic field lines.  
(4 marks)
- (d) Differentiate between solenoid and relay in terms of their construction and application.  
(4 marks)
- (e) Figure 1 shows a current-carrying conductor placed in a uniform magnetic field between two magnetic poles. The direction of current is into the page as indicated by the symbol ( $\otimes$ ). Discuss the rule used to determine the direction of force acting on the conductor and state the direction of motion of the conductor.

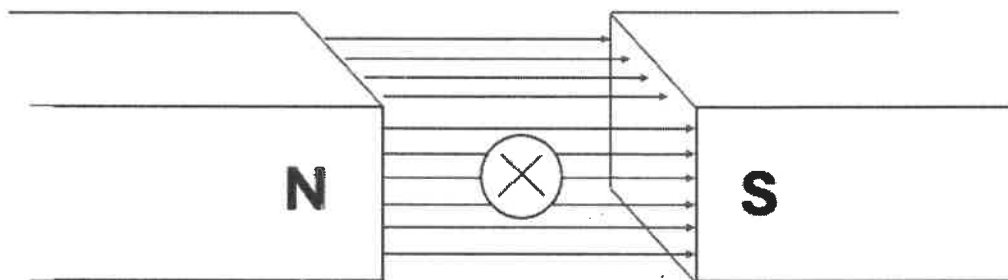


Figure 1

(4 marks)

## Question 2

- (a) Define electric voltage (potential difference) by using the mathematical relationship between voltage, energy, and charge.  
(4 marks)
- (b) Describe independent and dependent sources including **ONE (1)** example of each.  
(4 marks)
- (c) Describe the characteristics of conductors and insulators in terms of energy band gap and electrical resistance.  
(4 marks)
- (d) Differentiate between n-type and p-type semiconductor materials based on charge carriers and impurity doping.  
(4 marks)
- (e) Figure 2 illustrates the V-I characteristic curve of a p-n junction diode under forward bias. Explain the behaviour of the diode in the region after the knee voltage.

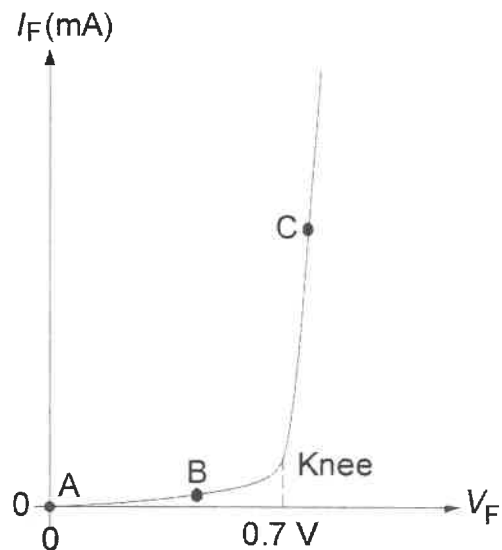


Figure 2

(4 marks)

**SECTION B (Total: 60 marks)**

**INSTRUCTION: Answer THREE (3) questions only.**

**Question 3**

- (a) For the circuit in Figure 3, determine the *equivalent resistance*,  $R_{eq}$  seen at terminals a–b.

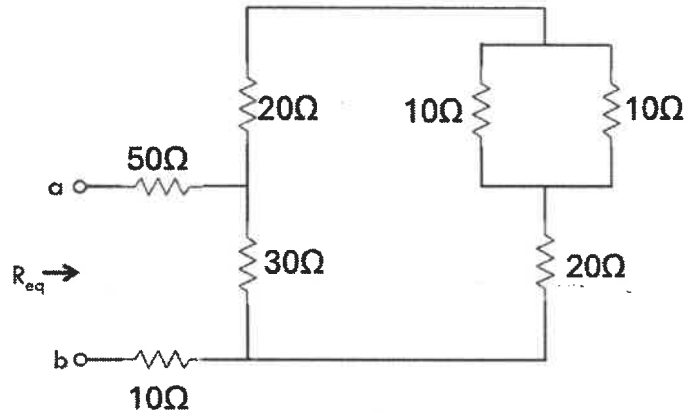


Figure 3

(8 marks)

- (b) Using *current division rule*, calculate currents  $i_1$  and  $i_2$  in the network shown in Figure 4.

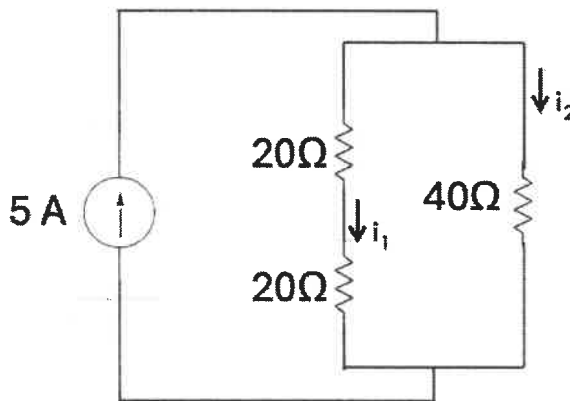


Figure 4

(6 marks)

- (c) Classify rectifiers according to their type of rectification using state their circuit configuration. (6 marks)

**Question 4**

- (a) Compute the total capacitance  $C_{eq}$  for the capacitor network in Figure 5.

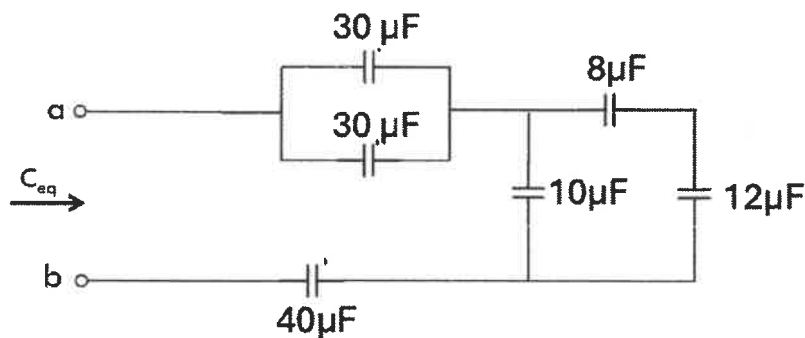


Figure 5

(8 marks)

- (b) In the circuit shown in Figure 6, determine  $V_o$  using voltage divider principle.

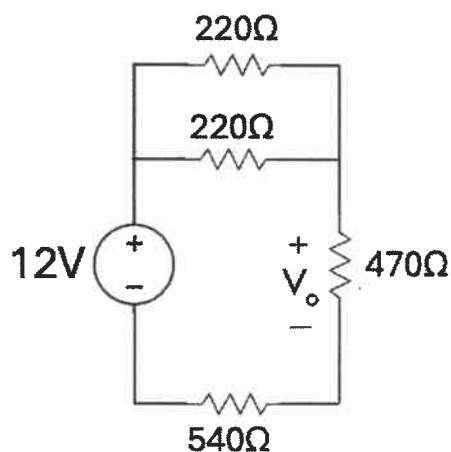


Figure 6

(6 marks)

- (c) Differentiate between positive clamper and negative clamper using suitable schematic diagrams, where the output waveform sketches are clearly shown.

(6 marks)

**Question 5**

- (a) Determine the equivalent inductance  $L_{eq}$  at terminals a–b for the network shown in Figure 7.

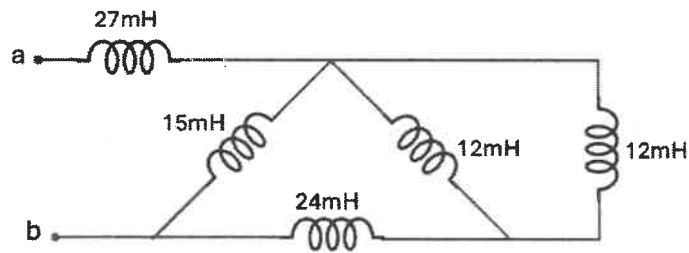


Figure 7

(8 marks)

- (b) For the circuit in Figure 8, calculate the loop current,  $i$ , by applying Kirchhoff's Voltage Law (KVL).

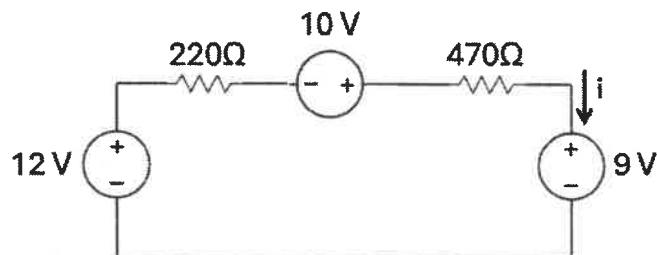


Figure 8

(6 marks)

- (c) Compare forward bias and reverse bias operation of a p–n junction diode by explaining the conduction behavior in each condition with reference to depletion layer and current flow.

(6 marks)

Question 6

- (a) According to the inductor circuit in Figure 9 under DC steady-state condition, calculate the current  $i_x$  flowing through the inductor.

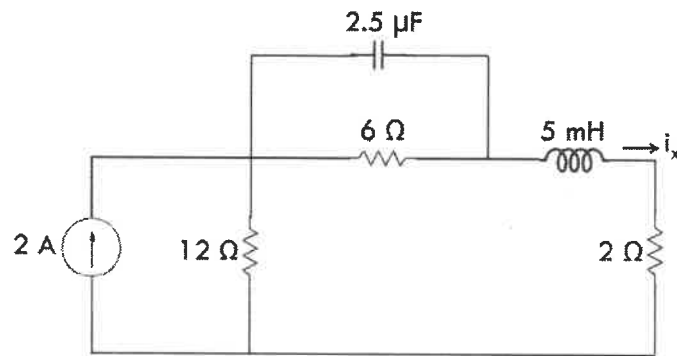


Figure 9

(8 marks)

- (b) For the network in Figure 10, determine  $i(t)$  for  $t > 0$ , assuming the switch (S1) was open for a long time and closes at  $t = 0$ . Given  $i_x(t) = i_x(0^+)e^{-t/\tau}$ .

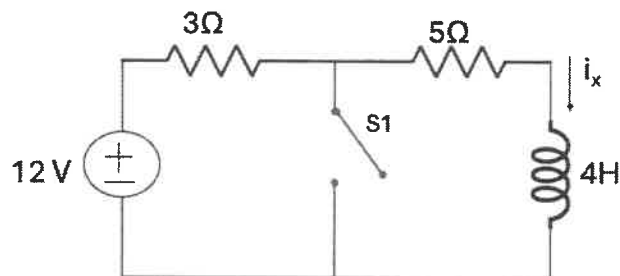


Figure 10

(6 marks)

- (c) Analyse the V-I characteristics of a p-n junction diode under forward bias and reverse bias.

## Question 7

(a) Figure 11 shows a silicon diode (0.7 V drop) connected in forward bias with a series resistor and DC supply. Determine:

- i. Diode current,  $I_D$
- ii. Voltage across the resistor,  $V_R$

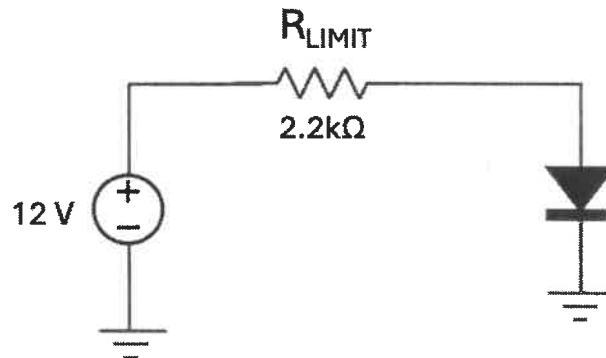


Figure 11

(8 marks)

(b) The diode in Figure 12 is now reverse biased with  $V_S = 10\text{ V}$ . Assume ideal diode reverse current  $\approx 0\text{ A}$ . Determine:

- i. Reverse current
- ii. Voltage across diode

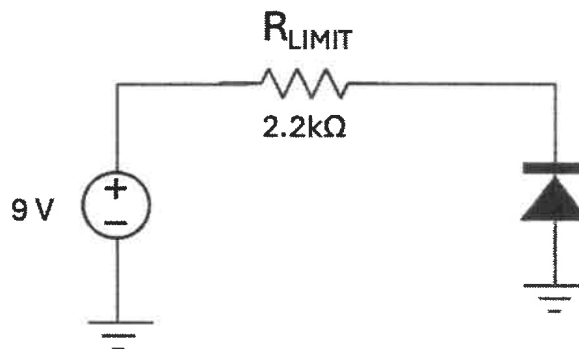


Figure 12

(6 marks)

(b) Differentiate between half-wave rectifier and full-wave rectifier in terms of:

- i. Circuit configuration
- ii. Efficiency of rectification
- iii. Output waveform characteristics

(6 marks)

END OF EXAMINATION PAPER

