



**UNIVERSITI KUALA LUMPUR**  
**Malaysian Institute of Marine Engineering Technology**

---

**FINAL EXAMINATION**  
**OCTOBER 2025 SEMESTER SESSION**

---

<b>SUBJECT CODE</b>	<b>: LEB31003</b>
<b>SUBJECT TITLE</b>	<b>: POWER ELECTRONICS</b>
<b>PROGRAMME NAME</b> (FOR MPU: PROGRAMME LEVEL)	<b>: BACHELOR OF ELECTRICAL AND ELECTRONICS ENGINEERING TECHNOLOGY (MARINE) WITH HONOURS</b>
<b>TIME / DURATION</b>	<b>: 09.00 AM - 12.00 PM (3 HOURS)</b>
<b>DATE</b>	<b>: 30 JANUARY 2026</b>

---

**INSTRUCTIONS TO CANDIDATES**

---

1. Please read **CAREFULLY** the instructions given in the question paper.
  2. This question paper has information printed on both sides of the paper.
  3. This question paper consists of **FIVE (5)** questions.
  4. Answer **FOUR (4)** questions **ONLY**.
  5. Please write your answers on this answer booklet provided.
  6. Answer **ALL** questions in English language **ONLY**.
  7. Answer should be written in blue or black.
  8. Formula is appended for your reference.
- 

**THERE ARE 3 PAGES OF QUESTIONS, EXCLUDING THIS PAGE.**

---

**INSTRUCTION: Answer FOUR (4) questions only**

**Please use the answer booklet provided**

**Question 1**

- a) The basic element of Power Electronic Technology is the power processor, which can be seen to provide a number of different conversions. Define power electronics. Give ONE application of power electronics and a list of THREE examples.

(5 marks)

- b) Describe the principle of power diodes and thyristors, then sketch the symbol on each component.

(8 marks)

- c) The controlled single-phase full-wave rectifier circuit of Figure 1 has a resistive load with  $R = 20\Omega$  and. The AC source is  $120 V_{rms}$  at  $60 Hz$  and delay angle is  $45^\circ$

Calculate:

- i) The average load current
- ii) The rms load voltage
- iii) The rms load current

(12 marks)

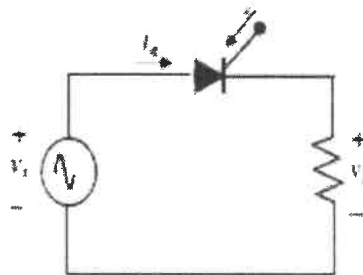


Figure 1

**Question 2**

- a) Input to the step-up chopper is  $200V$ . The output required is  $600V$ . If the conducting time of the thyristor is  $200 \mu sec$ , compute the chopping frequency.

(6 marks)

- b) If the pulse width is halved for a constant frequency of operation, determine the new output voltage.

(6 marks)

- b) DC chopper works on DC voltage as a step-up and step-down transformer. Briefly explain the principle of step-up and step-down DC choppers with R-L load of the transformer. [hint: Include together with the chopper circuit in answer]
- (13 marks)

**Question 3**

- a) List 5 characteristics of a good inverter and 5 applications of the inverter.
- (5 marks)
- b) Briefly explain the operation of a single-phase full-bridge inverter and sketch the waveform produced.
- (12 marks)
- c) The single-phase inverter is characterized by two distinct types of sources: the voltage source and the current source.
- i) Draw the circuit of a single-phase half-bridge inverter, which includes a voltage source, two diodes, and two thyristors using a suitable circuit.
- (4 marks)
- ii) Draw the circuit of the single -phase full bridge inverter, which consists of four diodes and 4 thyristors by using a suitable circuit.
- (4 marks)

**Question 4**

- a) Explain:
- i) the function of the buck-boost converter
- (5 marks)
- ii) the working principle of the buck converter
- (5 marks)

b) The buck-boost converter has the following parameters

$$V_s = 24V, D = 0.4, R = 10\Omega, L = 100\mu H, C = 400\mu F, F = 25kHz$$

Assuming ideal components, calculate;

- i. The output voltage  $V_o$  (4 marks)
- ii. The maximum and minimum inductor current (6 marks)
- iii. The output voltage ripple. (5 marks)

**Question 5**

- a) i) State the FOUR components of Power System that need to be protected. (2 marks)
- ii) List FOUR devices in the power protection system. (2 marks)
- iii) Briefly explain any TWO protective devices in the power system. (8 marks)
  
- b) A DC chopper has a resistive load of  $20\Omega$  and input voltage  $V_s = 220V$ . When chopper is ON, its voltage drop is 1.5 volts and chopping frequency is 10KHz. If the duty cycle is 80%, determine the average output voltage and the chopper on time. (7 marks)
  
- c) If the chopper circuit is operating on TRC at a frequency of 2KH on a 460V supply and the load voltage is 350V, calculate the conduction period of the thyristor in each cycle. (6 marks)

END OF EXAMINATION PAPER

## FORMULAS -LEB 31003

### FUNDAMENTALS OF AC

$$I = I_0 \sin \omega t$$

$$V = V_0 \sin \omega t$$

$$I_{RMS} = \frac{I_0}{\sqrt{2}} = 0.707I_0$$

$$V_{RMS} = \frac{V_0}{\sqrt{2}} = 0.707V_0$$

$$Z = \frac{V_{RMS}}{I_{RMS}} = \frac{V_0}{I_0} = R$$

### PURELY INDUCTIVE, L

$$\Delta\phi = \left(\omega t + \frac{\pi}{2}\right) - \omega t$$

$$\Delta\phi = \frac{\pi}{2} \text{ rad} = 90^\circ$$

$$X_L = 2\pi fL$$

### RCL SERIES

$$V = IZ$$

$$\frac{V}{I} = Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

### POWER OF PURELY RESISTIVE SERIES, R

$$P = (I_0 \sin \omega t)(V_0 \sin \omega t)$$

$$P = I_0 V_0 \sin^2 \omega t$$

$$P = \frac{I_0 V_0}{2} - \frac{I_0 V_0 \cos 2\omega t}{2}$$

$$P = \left(\frac{I_0}{\sqrt{2}} \cdot \frac{V_0}{\sqrt{2}}\right) - \left(\frac{I_0}{\sqrt{2}} \cdot \frac{V_0}{\sqrt{2}} \cdot \cos 2\omega t\right)$$

### POWER OF PURELY CAPACITIVE SERIES, C

$$P = IV$$

$$P = (I_0 \cos \omega t)(V_0 \sin \omega t)$$

$$P = \frac{I_0 V_0}{2} \sin 2\omega t$$

### POWER OF R, RC, RL AND RCL

$$P_{av} = I_{RMS} V_{R,RMS}$$

$$\cos \phi = \frac{V_R}{V}$$

$$V_R = V \cos \phi$$

$$P_{av} = I_{RMS} V_{RMS} \cos \phi$$

### PURELY RESISTIVE, R

$$Z = \frac{V_{RMS}}{I_{RMS}} = \frac{V_0}{I_0} = R$$

### PURELY CAPACITIVE, C

$$\Delta\phi = \omega t - \left(\omega t + \frac{\pi}{2}\right)$$

$$\Delta\phi = -\frac{\pi}{2} \text{ rad} = -90^\circ$$

$$X_C = \frac{1}{2\pi fC}$$

### BOTH RC AND RL SERIES

$$V = IZ$$

$$\frac{V}{I} = Z = \sqrt{R^2 + X_{[C/L]}^2}$$

$$\tan \phi = \frac{V_{[C/L]}}{V_R}$$

### RESONANCE FREQUENCY

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

### POWER

$$P = IV$$

$$P_f = \cos \phi$$

$$P_{av} = P \cdot P_f = IV \cos \phi$$

$$P = (I_{RMS} V_{RMS}) - (I_{RMS} V_{RMS} \cos 2\omega t)$$

$$P_{av} = \frac{I_0 V_0}{2} = I_{RMS} V_{RMS}$$

### POWER OF PURELY INDUCTIVE SERIES, L

$$P = (I_0 \sin \omega t)(V_0 \cos \omega t)$$

$$P = \frac{I_0 V_0}{2} \sin 2\omega t$$

$$P_{av} = 0$$

### POWER FACTOR OF R, RC, RL AND RCL

$$P_f = \cos \phi = \frac{P_R}{I^2 Z}$$

$$P_f = \cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z}$$

$$P_r = \text{Average Real Power}, \quad P_{av} = I^2 Z \cos \phi = P_r$$

## HALF-WAVE RECTIFIER

$$V_o = \frac{V_m}{\pi}$$

$$I_o = \frac{V_o}{R} = \frac{V_m}{\pi R}$$

$$V_{RMS} = \frac{V_m}{2}$$

$$I_{RMS} = \frac{V_m}{2R}$$

## FULL-WAVE RECTIFIER

$$V_o = \frac{2V_m}{\pi}$$

$$I_o = \frac{V_o}{R} = \frac{2V_m}{\pi R}$$

$$V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$I_o = \frac{V_o}{R} = \frac{V_m}{\pi R} (1 + \cos \alpha)$$

$$I_{RMS} = \frac{V_m}{R} \sqrt{\frac{1}{2} - \frac{\alpha}{2\pi} + \frac{\sin(2\alpha)}{4\pi}}$$

$$I_{S,RMS} = I_{o,RMS}$$

$$i_o(\omega t) = \frac{V_m}{Z} [\sin(\omega t - \theta) - \sin(\alpha - \theta)e^{-(\omega t - \alpha)/\tau}]$$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

$$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$\tau = \frac{L}{R}$$

➤ On-Off control

- Output load voltage

$$V_o - rms = V_s \sqrt{\frac{n}{m+n}} = V_s \sqrt{k}$$

\*k is duty cycle

➤ Phase control

- rms value output voltage

$$V_o = V_s \left[ \frac{1}{2\pi} (2\pi - \alpha + \frac{\sin 2\alpha}{2}) \right]^{1/2}$$

- average value output voltage

$$V_o = \frac{\sqrt{2}V_s}{2\pi} (\cos \alpha - 1)$$

## BUCK AND BOOST CONVERTER

$$V_o = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$I_{o,RMS} = \frac{V_{o,RMS}}{R}$$

$$pf = \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$I_{SCR,avg} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

$$I_{rms,scr} = \frac{I_{o,RMS}}{\sqrt{2}}$$

$$V_o = \frac{V_s}{1-D}$$

$$I_L = \frac{V_s}{(1-D)^2 R}$$

$$I_{max} = \frac{V_s}{(1-D)^2 R} + \frac{V_s DT}{2L}$$

$$I_{min} = \frac{V_s}{(1-D)^2 R} - \frac{V_s DT}{2L}$$

$$\frac{\Delta_o}{V_o} = \frac{D}{RCF}$$

$$I_D = I_o = \frac{V_o}{R}$$

- RMS OUTPUT VOLTAGE

$$V_{orms} = \frac{V_m}{\sqrt{2}} \sqrt{1 - \frac{\alpha}{\pi} + \frac{\sin(2\alpha)}{2\pi}}$$

$$V_{orms} = \sqrt{PR}$$

$$I_{rms} = \frac{V_{orms}}{R}$$

- POWER FACTOR OF THE LOAD

$$PF = \frac{P}{S}$$

- RMS SCR CURRENT

$$I_{scr,rms} = \frac{I_{o,rms}}{\sqrt{2}}$$

- AVERAGE SCR CURRENT

$$I_{scr,avg} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$$

