



UNIVERSITI KUALA LUMPUR
MALAYSIAN INSTITUTE OF MARINE ENGINEERING TECHNOLOGY

FINAL EXAMINATION
JANUARY 2016 SEMESTER

COURSE CODE : LEB10603
COURSE NAME : ANALOGUE ELECTRONICS
PROGRAMME NAME : BACHELOR OF ENGINEERING TECHNOLOGY IN
(FOR MPU: PROGRAMME LEVEL) MARINE ELECTRICAL AND ELECTRONICS
DATE :
TIME :
DURATION : 3 HOURS

INSTRUCTIONS TO CANDIDATES

NOTE: Instructions below to be edited to suit the needs of the intended course/examination.

1. Please **CAREFULLY** read the instructions given in the question paper.
2. This question paper has information printed on both sides of the paper.
3. This question paper consists of **TWO (2)** sections; Section A and Section B.
4. Answer **ALL** questions in Section A. For Section B, answer **THREE (3)** questions.
5. Please write your answers on the **OMR** answer script and answer booklet provided.
6. Answer all questions in **English** language **ONLY**.

THERE ARE 5 PAGES OF QUESTIONS, INCLUDING THIS PAGE.

SECTION B (Total: 40 marks)

INSTRUCTION: Answer ALL questions.

Please use the answer booklet provided.

Question 1

- (a) Describe how DC current gain (β_{DC}) varies with temperature and collector current.
(Course Learning Outcome: 1)
(7 marks)
- (b) Discuss the operation of light-operated relay circuit as an example of phototransistor application. (Course Learning Outcome: 1)
(13 marks)

Question 2

Analyse the circuit shown Figure 2A and if the multistage is driven by 80Ω , $50\mu V$ source and the second stage is loaded with an $R_L = 20k\Omega$, determine:

- i. voltage gain of each stage
(12 marks)
- ii. overall voltage gain
(5 marks)
- iii. express the gains found in Question (i) and Question (ii).
(3 marks)

(Course Learning Outcome 2)

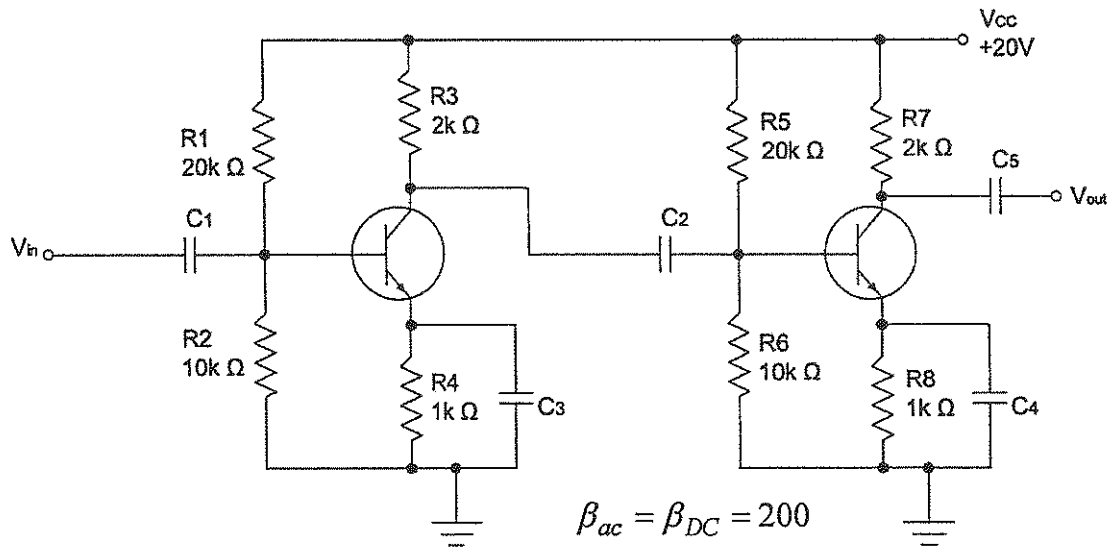


Figure 2A

SECTION B (Total: 60 marks)

INSTRUCTION: Answer THREE (3) questions ONLY.

Please use the answer booklet provided.

Question 3

Develop an alarm system circuit for detecting forced entry into a building using transistor switches. The alarm system will accommodate four zones with any number of openings. It can be expanded to cover additional zones. For the purpose of this application, a zone is one room in a house or other building. The sensor used for each opening can be mechanical switch, a magnetically operated switch, or an optical sensor. Detection of intrusion can be used to initiate an audible alarm signal and/or to initiate transmission of a signal over the phone line to a monitoring service. You are required to explain in detail the process of circuit construction.

(Course Learning Outcome 1 & 2)

(20 marks)

Question 4

Class AB power amplifier application in the PA system are simplified using the block diagram as shown in Figure 4A. In this application, the power amplifier is constructed using a circuit in Figure 4B and assumed audio preamp output voltage is 10Vpp. Analyse the amplifier circuit given (Figure 4B) in order to identify the following information:

- i. The DC parameters $V_{B(Q1)}, V_{B(Q2)}, V_E, I_{CQ}, V_{CEQ(Q1)}, V_{CEQ(Q2)}$.
(9 marks)
- ii. Determine the power delivered to the 50Ω speaker.
(4 marks)
- iii. Sketch the load line for the npn transistor and label the saturation current and show the Q-point.
(7 marks)

(Course Learning Outcome 2)

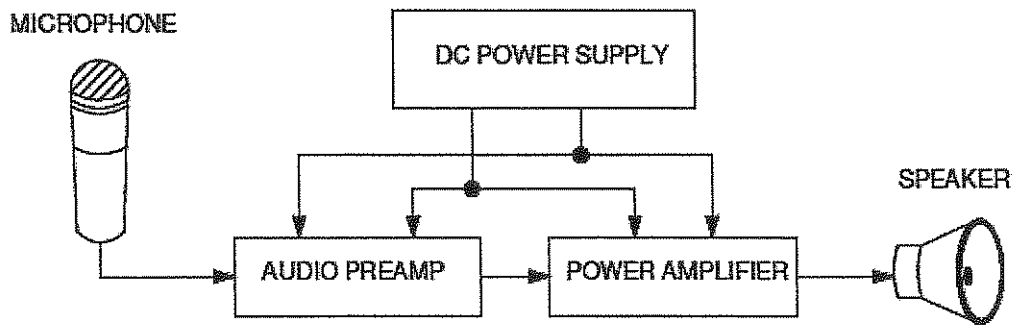


Figure 4A

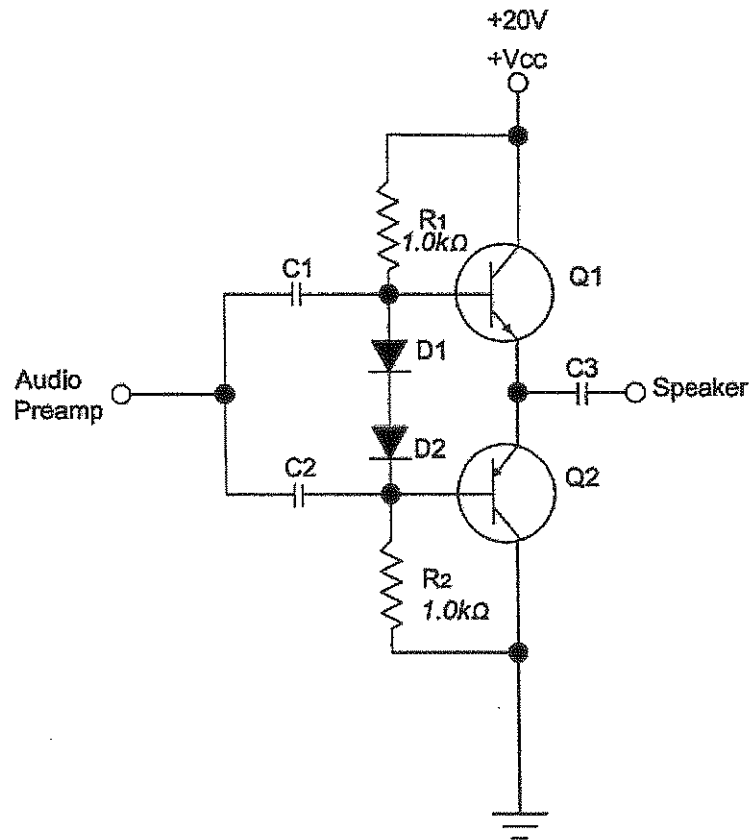


Figure 4B

Question 5

Design a circuit using an n-channel E-MOSFET with the following datasheet specifications: $I_{D(on)} = 500mA @ V_{GS} = 10V$ and $V_{GS(th)} = 1V$. Use a +15V dc supply voltage with voltage divider bias. The voltage at the drain with respect to ground is to be +10V. The maximum current from the supply is to be 25mA.

(Course Learning Outcome 1 & 2)

(20 marks)

Question 6

- (a) Compare a practical operational amplifier with ideal operational amplifier. (6 marks)
- (b) Compare the general effects operational amplifier with negative feedback and without negative feedback. (7 marks)
- (c) Determine the output voltage waveform as shown in Figure 6A. (7 marks)

(Course Learning Outcome 1 & 2)

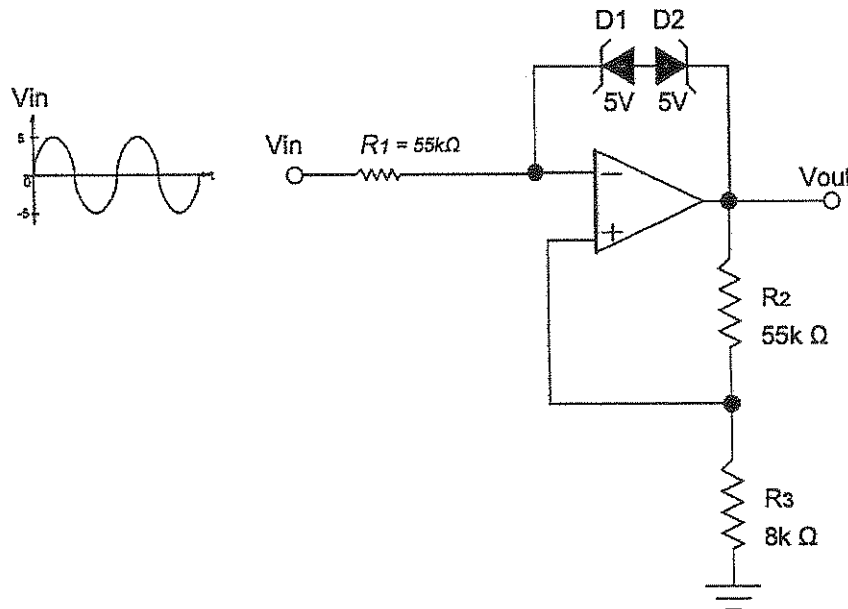


Figure 6A

END OF EXAMINATION PAPER

